



# **B38DB: Digital Design and Programming**

## **Sequential Logic Design – Flip Fops**

**Mustafa Suphi Erden**

Heriot-Watt University  
School of Engineering & Physical Sciences  
Electrical, Electronic and Computer Engineering  
Room: EM 2.01  
Phone: 0131-4514159  
E-mail: [m.s.erden@hw.ac.uk](mailto:m.s.erden@hw.ac.uk)

# Introduction

  

## ■ Sequential circuit


- Output depends not only on present inputs, but also on the circuit's present **state**, which is all the bits currently **stored** in the circuit and **depends on the past sequence of inputs**.

## ■ We will:

- Design a new building block, a **flip-flop**, that stores one bit
- Combine that block to build multi-bit storage **register**
- Describe the sequential behavior using a **finite state machine (FSM)**
- Convert a FSM to a **controller** – a sequential circuit having a register and combinational logic

 
# Example: Bit Storage

- Flight attendant call button
  - Press call: light turns on
    - **Stays on** after button released
  - Press cancel: light turns off
  - Logic gate circuit to implement this?




Doesn't work.  $Q=1$  when  $\text{Call}=1$ , but doesn't stay 1 when  $\text{Call}$  returns to 0

 
*We need some form of “feedback” in the circuit*



1. Call button pressed – light turns on

 


 
2. Call button released – light **stays on**



3. Cancel button pressed – light turns off
  
# First Attempt at Bit Storage





- We need some sort of feedback
  - Does the circuit on the right do what we want?



- No: Once Q becomes 1 (when S=1), Q stays 1 forever – no value of S can bring Q back to 0

    
# Bit Storage Using an SR Latch

- Does the circuit on the right, with cross-coupled NOR gates, do what we want?
  - Yes!



 
## Example: Using SR Latch for Bit Storage

- SR latch can serve as bit storage as in the previous example of flight-attendant call button
  - Call=1 : sets Q to 1
    - Q stays 1 even after Call=0
  - Cancel=1 : resets Q to 0




- But, there's a problem...

 


## Problem with SR Latch

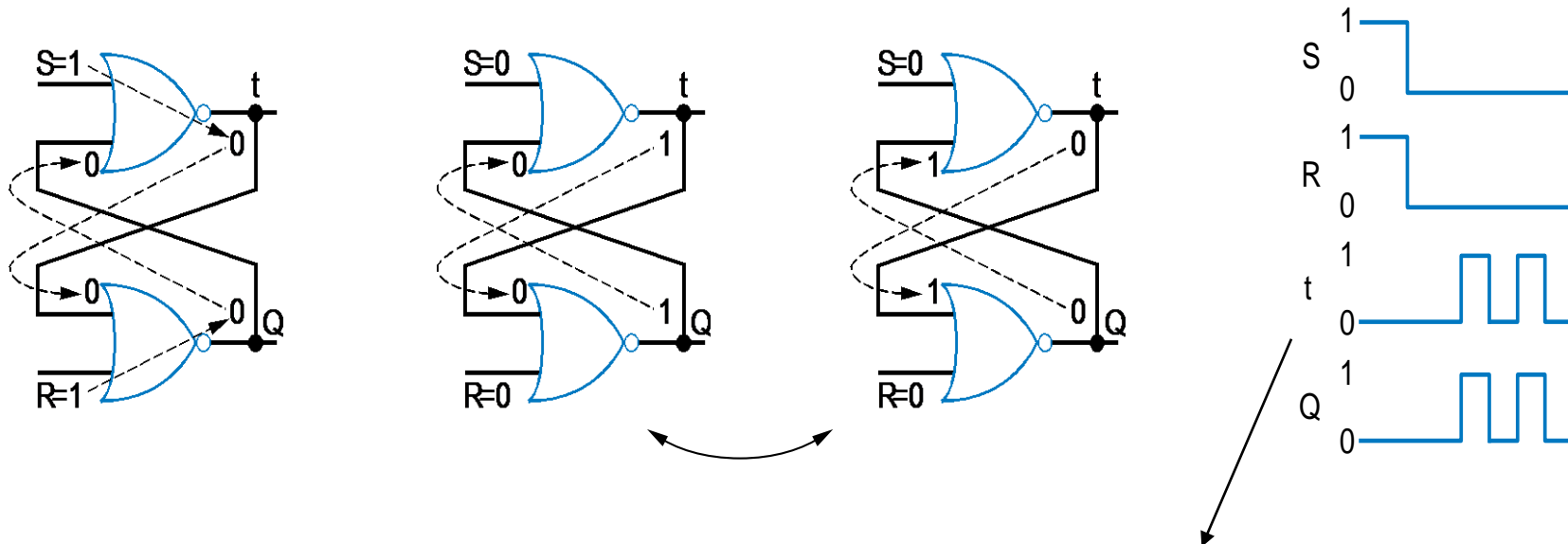- Problem

- If  $S=1$  and  $R=1$  simultaneously, we don't know what value  $Q$  will take.




 Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which.



 
# Problem with SR Latch

- This problem can occur even if SR inputs come from a circuit that supposedly never sets  $S=1$  and  $R=1$  at the same time
- It happens due to different delays of different paths






 
The longer path from X to R than to S might result  $SR=11$  for short time – could be long enough to cause oscillations




  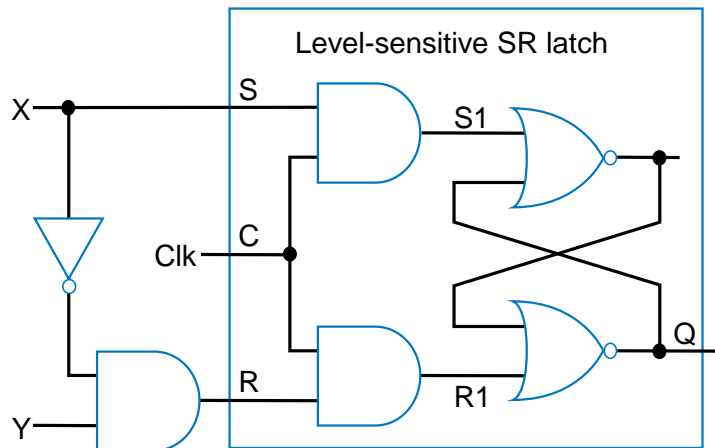 
# Solution: Level-Sensitive SR Latch



- Add enable input “C” as shown
  - Only let S and R change when  $C=0$
  - Change C to 1 only after sufficient time for S and R to be stable



Level-sensitive  
SR latch symbol
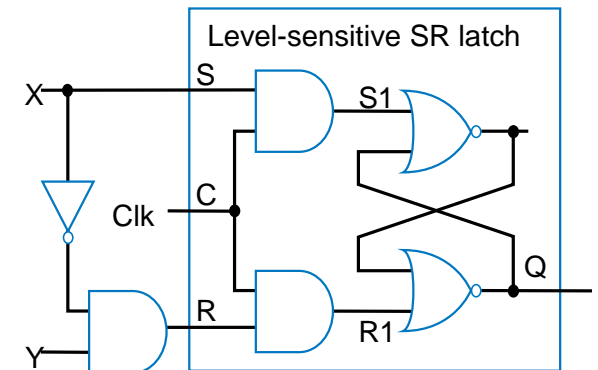 
# Clock Signals for a Latch

- How to choose the timing to set  $C=1$ ?
  - Most common solution → make  $C$  a pulse signal going up and down
    - $C=0$ : Safe to change  $X, Y$
    - $C=1$ : Must *not* change  $X, Y$
  - **Clock** signal – A pulsing signal used to enable latches
  - Sequential circuit storage components all use clock signals:
    - **synchronous** circuit → Most common type sequential circuit
    - asynchronous circuits – important topic, but left for advanced courses



# Clocks

- **Clock period:** time interval between pulses

- The signal below: period = 20 ns


- **Clock cycle:** one such time interval

- The signal below shows 3.5 clock cycles

- **Clock frequency:** 1/period




- The signal below: frequency =  $1 / 20 \text{ ns} = 50 \text{ MHz}$

Freq	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

 
   
# Level-Sensitive D Latch



- SR latch requires careful design to ensure  $SR=11$  never occurs
- D latch relieves designer of that burden
  - An inverter ensures R is always the opposite of S



D latch symbol

 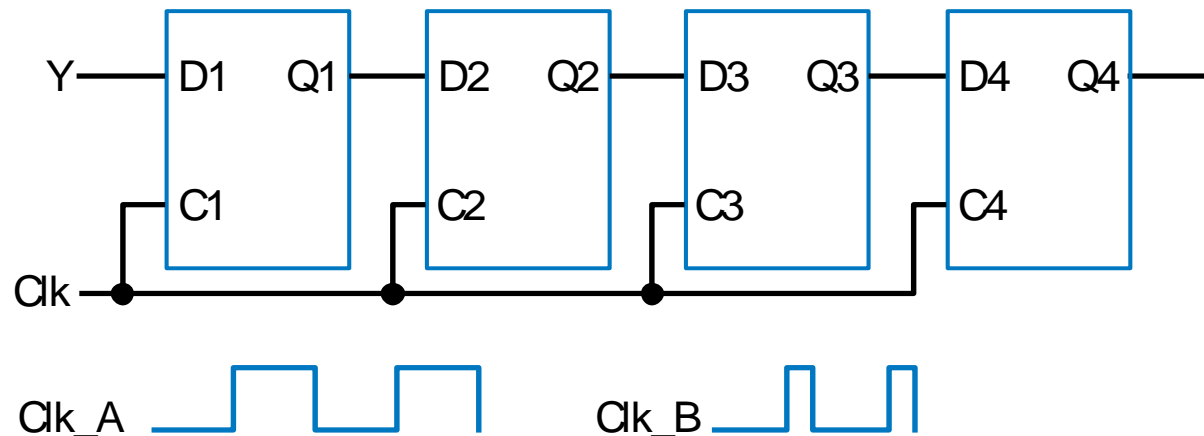
# Problem with Level-Sensitive D Latch

- D latch still has problem (as does SR latch)
  - When  $C=1$ , through how many latches will a signal travel?
  - Depends on for how long  $C=1$  holds
    - Clk\_A - signal may travel through multiple latches
    - Clk\_B - signal may travel through fewer latches
  - Can we design a bit storage that stores a value only on the **rising edge** of a clock signal?




 
# D Flip-Flop (1/3)




- **Flip-flop**: Bit storage that stores on clock edge, not level
- “Master-servant” design
  - Two latches → output of the first goes to the input of the second, with the first latch having inverted clock signal
  - “Master latch” loaded when  $C=0$ , servant loaded when  $C=1$
  - When  $C$  changes from 0 to 1, master is disabled, servant is loaded with the value that was at  $D$  just before  $C$  changed – i.e., with the value at  $D$  during the rising of  $C$



 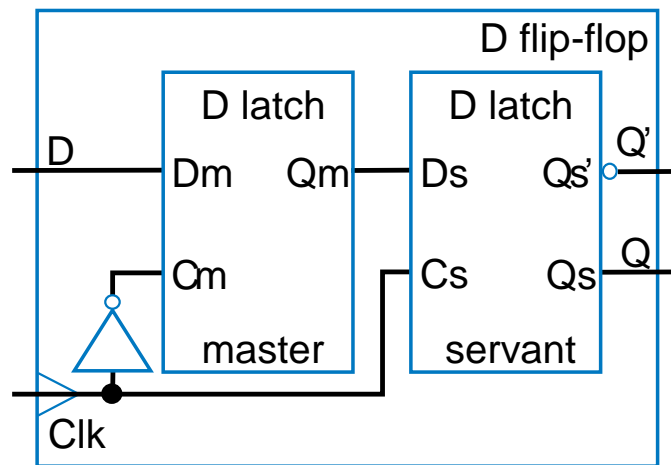
*Note: Hundreds of different flip-flop designs exist*



# D Flip-Flop (2/3)

 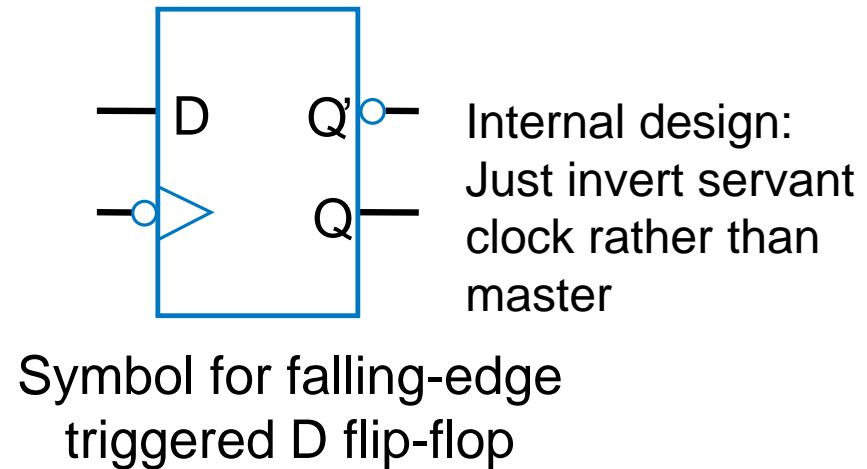 


## D Flip-Flop (3/3)

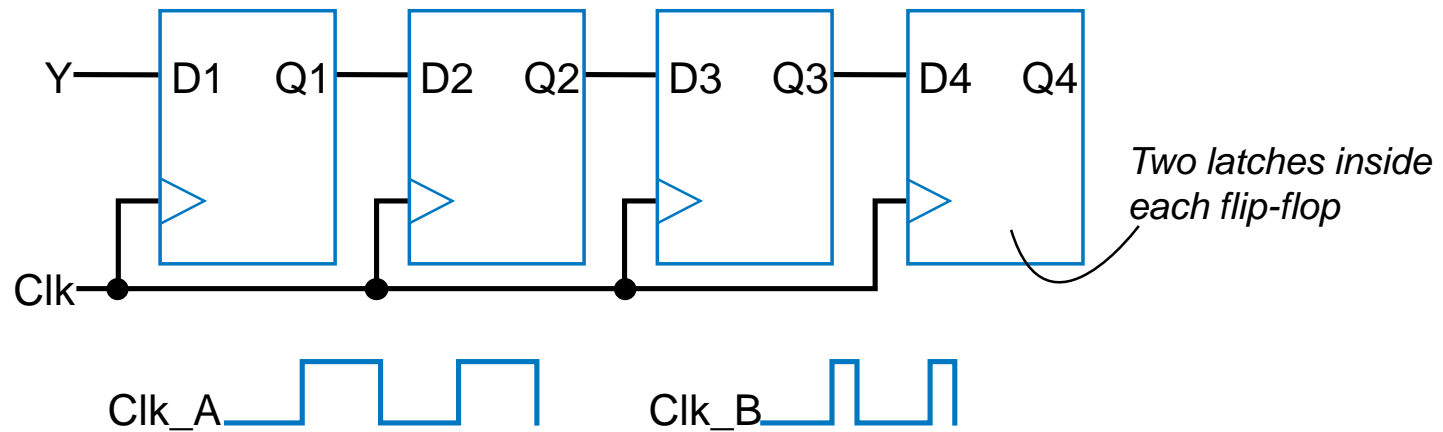

- The signal travels **through exactly one flip-flop**, for Clk\_A or Clk\_B
- On rising edge of Clk, all four flip-flops are loaded simultaneously and then they do not pay attention to their input, until the next rising edge.
- Doesn't matter how long Clk signal stays at level 1.




# D Latch vs. D Flip-Flop

 


- **Latch** is level-sensitive: Stores D when C=1
- **Flip-flop** is edge triggered: Stores D when C changes from 0 to 1


# Bit Storage Summary

 

 
**Feature:**  $S=1$  sets  $Q$  to 1,  $R=1$  resets  $Q$  to 0.  
**Problem:**  $SR=11$  yield undefined  $Q$ .



 **Feature:**  $S$  and  $R$  only have effect when  $C=1$ . We can design outside circuit so  $SR=11$  never happens when  $C=1$ .  
**Problem:** avoiding  $SR=11$  can be a burden.



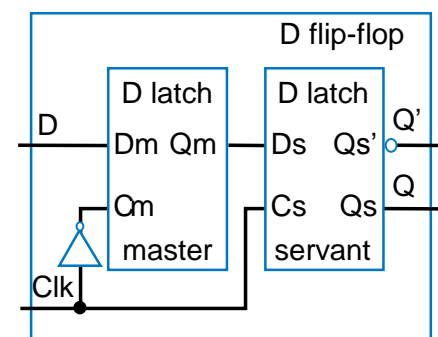**Feature:**  $SR$  can't be 11 if  $D$  is stable before and while  $C=1$ , and will be 11 for only a brief glitch even if  $D$  changes while  $C=1$ .  
**Problem:**  $C=1$  too long propagates new values through too many latches: too short may not enable a store.



**Feature:** Only loads  $D$  value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle. Tradeoff: uses more gates internally than  $D$  latch, and requires more external gates than  $SR$  – but gate count is less of an issue today.

- We considered increasingly better bit storage until we arrived at the robust  $D$  flip-flop bit storage