

# **B38DB: Digital Design and Programming**

## **Datapath Components – Registers**


**Mustafa Suphi Erden**

Heriot-Watt University  
School of Engineering & Physical Sciences  
Electrical, Electronic and Computer Engineering  
Room: EM 2.01  
Phone: 0131-4514159  
E-mail: [m.s.erden@hw.ac.uk](mailto:m.s.erden@hw.ac.uk)

# Introduction

- Up to now we learned about increasingly complex digital building blocks
  - Gates, multiplexors, decoders, basic registers, and controllers
- Controllers are good for systems with control inputs/outputs
  - **Control** input: Single bit (or just a few), representing environment event or state
    - e.g., 1 bit representing button pressed
  - **Data** input: Multiple bits collectively representing single entity
    - e.g., 7 bits representing temperature in binary
- We need building blocks for data processing
  - **Datapath components**, in other words **register-transfer-level (RTL) components**, to store/transform data
    - Put datapath components together to form a **datapath**


# Registers

 

*Basic register loads on every clock cycle.*


*How to control the loading to happen only when it is desired?*

# Register with Parallel Load

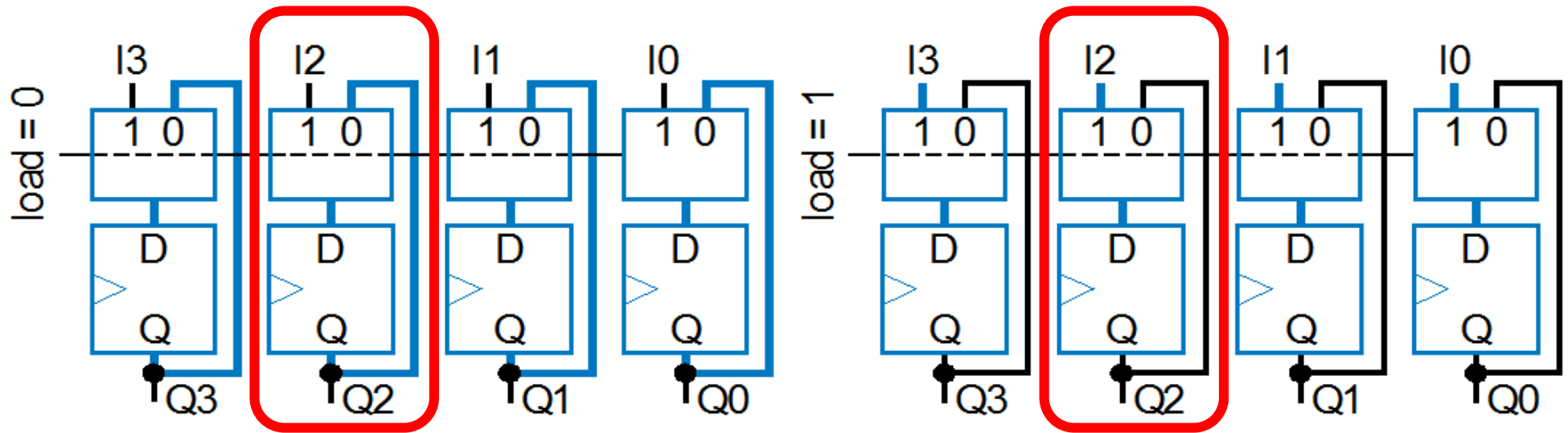


- Add 2x1 Mux to the front of each flip-flop
- Register's load input selects Mux input to pass
  - Either the existing flip-flop value, or a new value is loaded
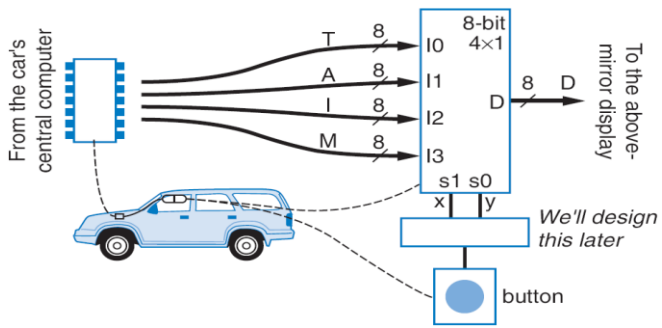
## Register Example: Above-Mirror Display







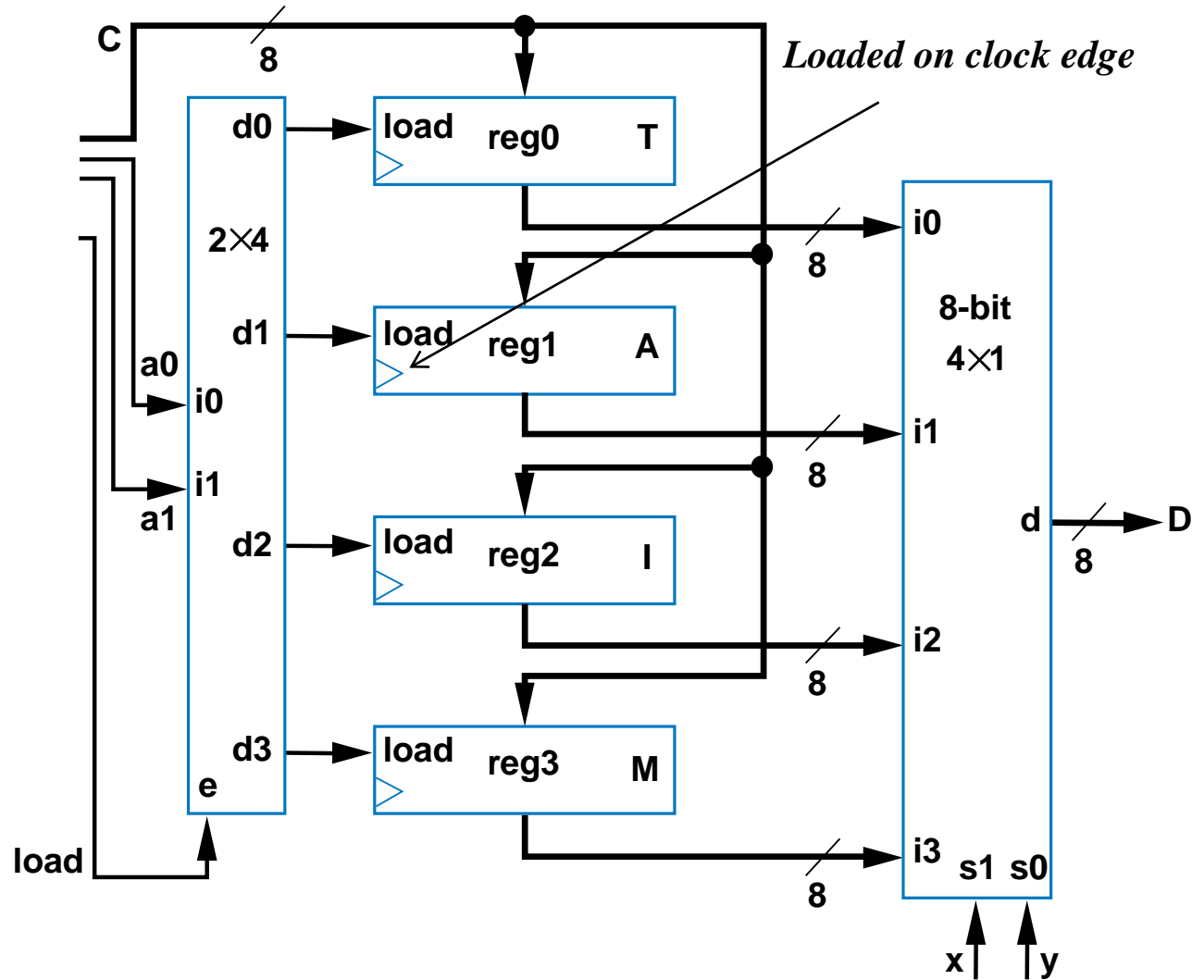- Initial design: Four simultaneous values from car's computer
- To reduce wires: Computer writes only 1 value at a time, loads into one of the four registers
  - Was:  $8+8+8+8 = 32$  wires
  - Now:  **$8+2+1 = 11$**  wires



    
# Shift Register

- Shift right
  - Move each bit one position right
  - Shift in 0 to leftmost bit



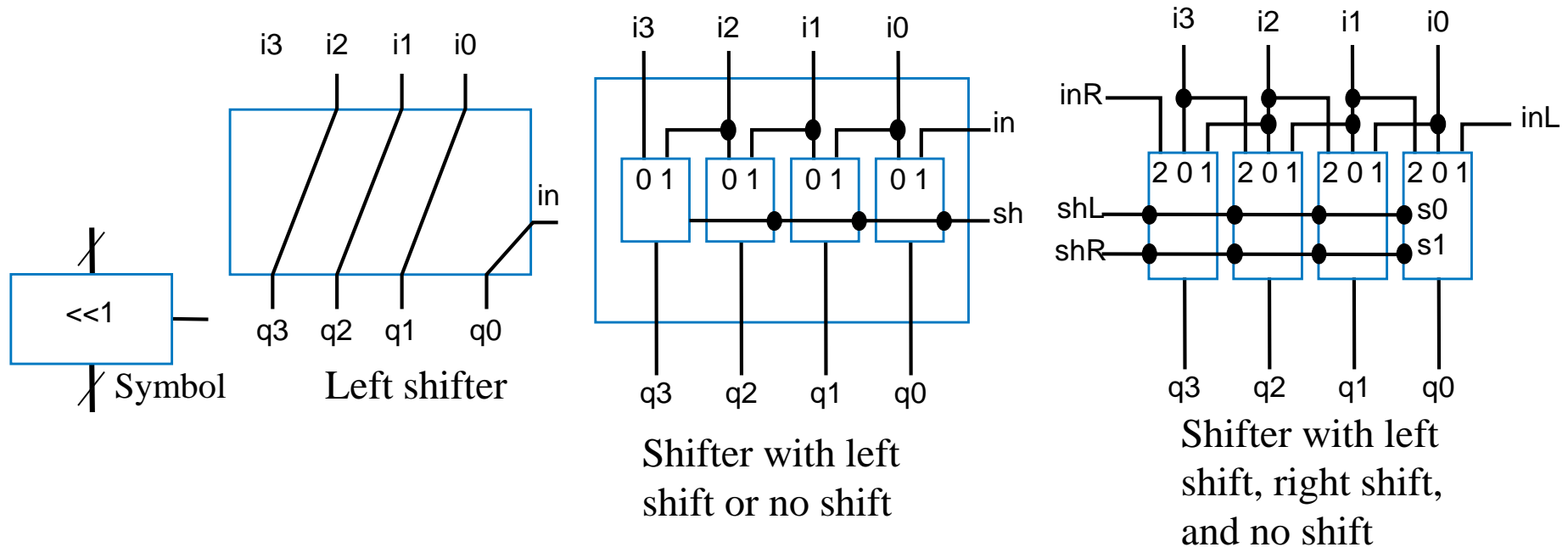
# Shifters

- Shifting (e.g., left shifting 0011 yields 0110) useful for:
  - Manipulating bits
  - Converting serial data to parallel (remember earlier above-mirror display example with shift registers)
  - Shift left once is same as multiplying by 2 (0011 (3) becomes 0110 (6))
  - Shifting right once is the same as dividing by 2


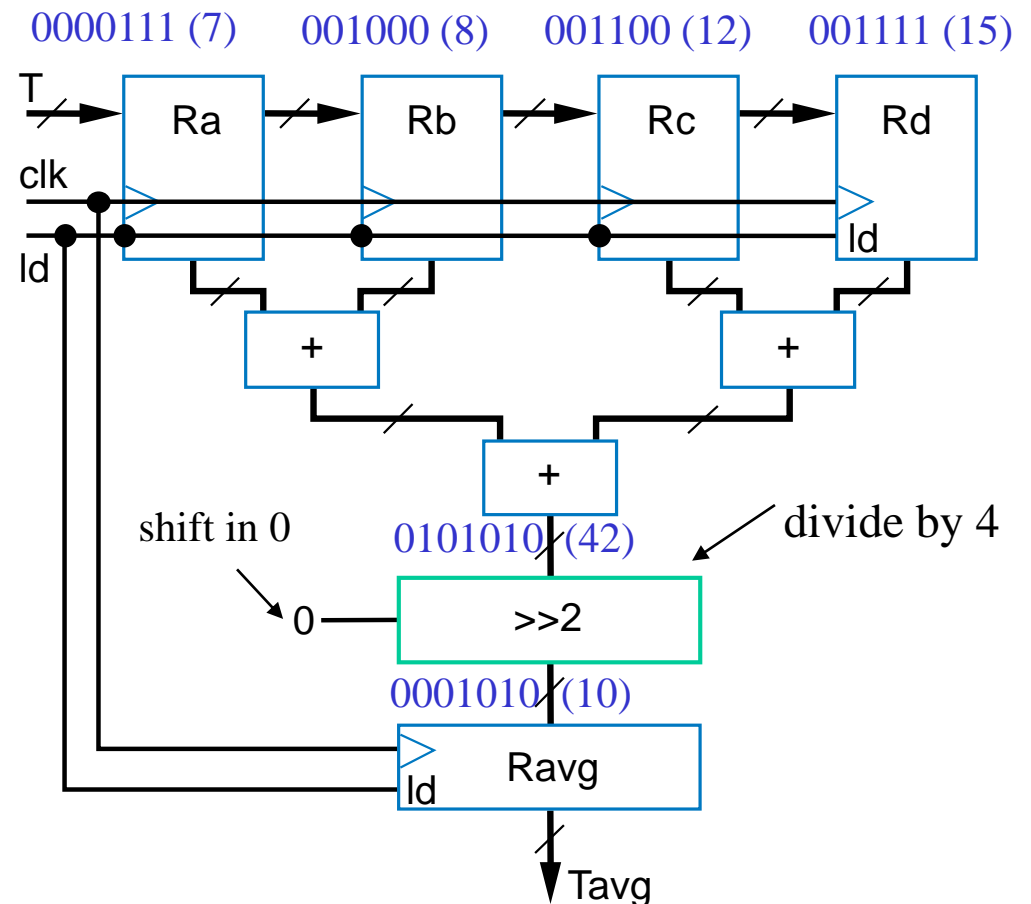
# Shifter Example: Temperature Averager

- Four registers storing a history of temperatures
- Want to output the average of those temperatures
- Add, then divide by four
  - Same as shift right by 2
  - Use three adders, and right shift by two






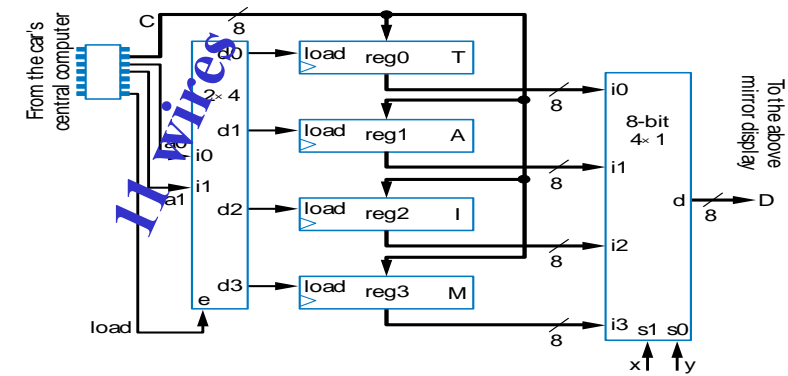
# Shift Register Example: Above-Mirror Display

- Earlier example:  
 $8 + 2 + 1 = 11$  wires  
 from car's computer to  
 above-mirror display

- Use shift registers
  - Wires:  $1 + 2 + 1 = 4$**
  - Computer sends  
 one value at a time,  
 one bit per clock  
 cycle




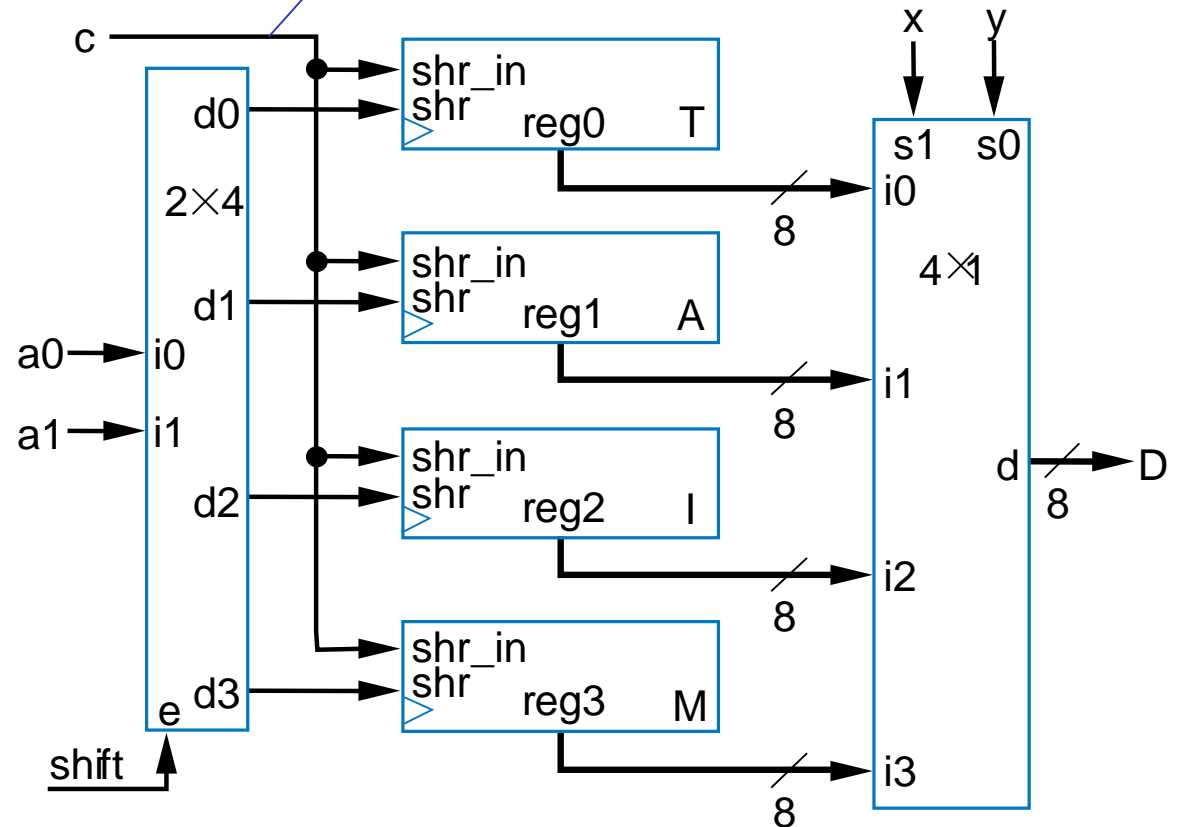Note: this line is 1 bit, rather than 8 bits as before


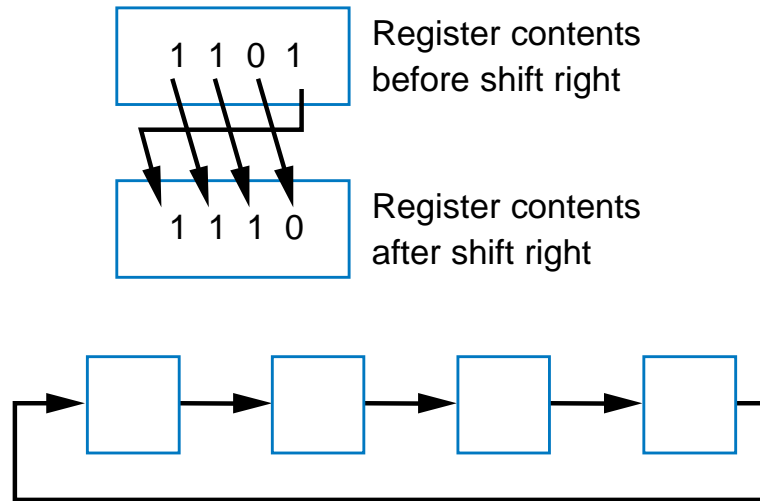
# Rotate Register

- Rotate right: leftmost bit comes from rightmost bit





Work out the actual connections with flip-flops and multiplexers!

# Multifunction Registers

Operation Table:

s1	s0	Operation
0	0	Maintain present value
0	1	Parallel load
1	0	Shift right
1	1	Shift left

 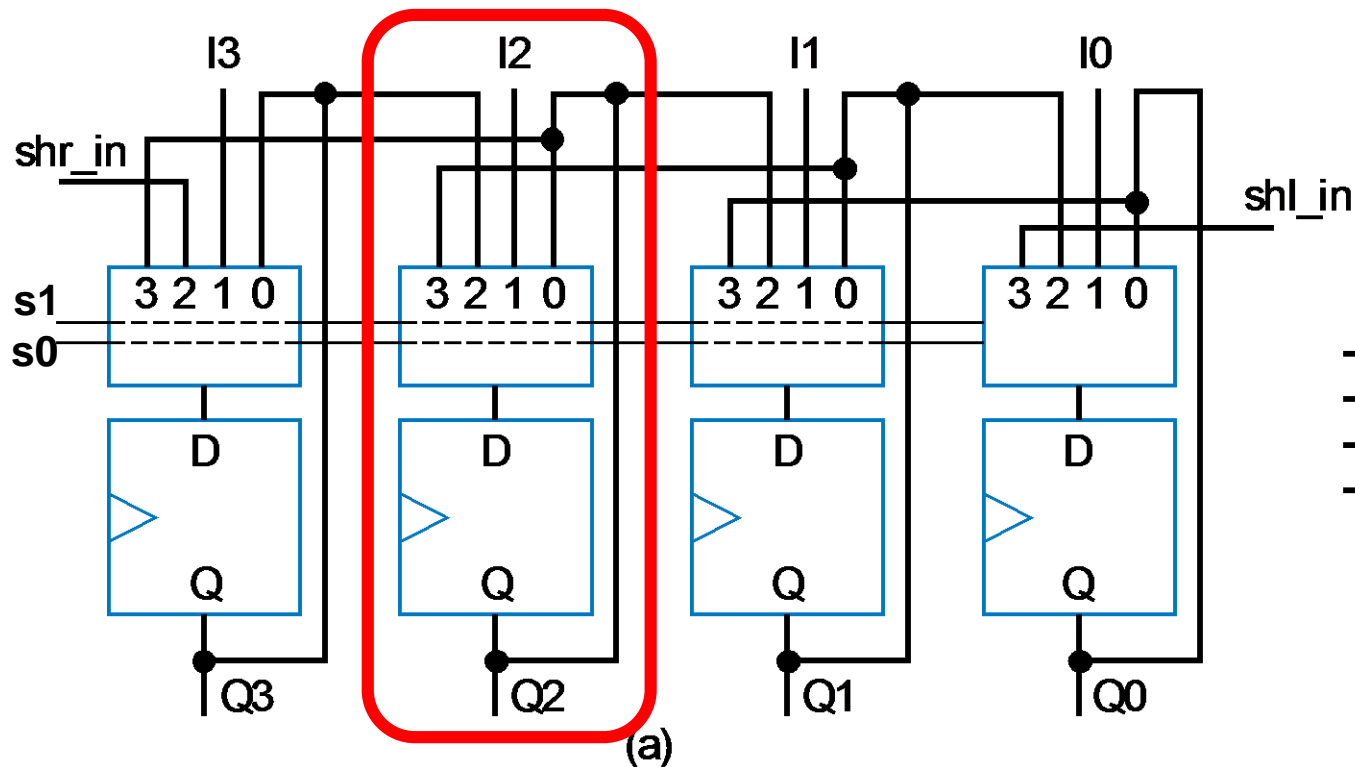


# Multifunction Registers with Separate Control Inputs

ld	shr	shl	Operation
0	0	0	Maintain present value
0	0	1	Shift left
0	1	0	Shift right
0	1	1	Shift right – shr has priority over shl
1	0	0	Parallel load
1	0	1	Parallel load – ld has priority
1	1	0	Parallel load – ld has priority
1	1	1	Parallel load – ld has priority

Truth table for combinational circuit

Inputs			Outputs		Operation
ld	shr	shl	s1	s0	
0	0	0	0	0	Maintain value
0	0	1	1	1	Shift left
0	1	0	1	0	Shift right
0	1	1	1	0	Shift right
1	0	0	0	1	Parallel load
1	0	1	0	1	Parallel load
1	1	0	0	1	Parallel load
1	1	1	0	1	Parallel load

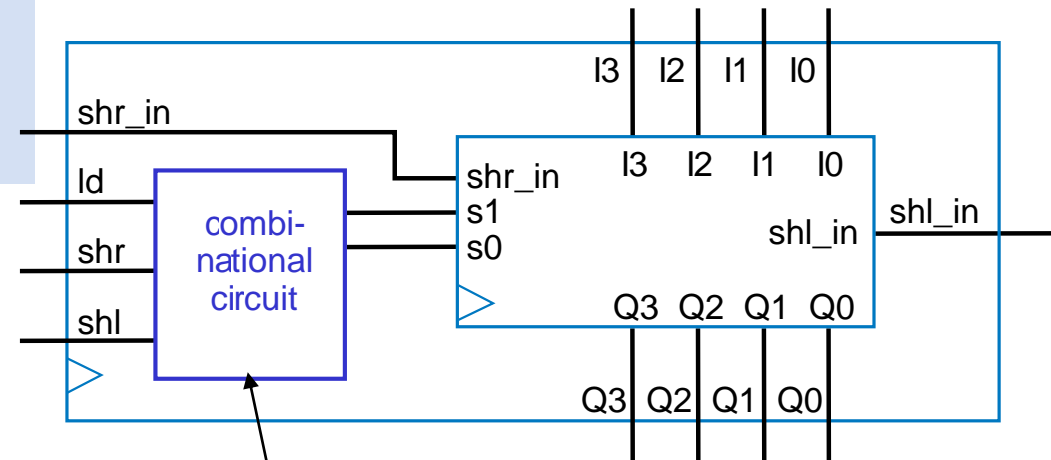

$$s1 = ld' \cdot shr' \cdot shl + ld' \cdot shr \cdot shl' + ld' \cdot shr \cdot shl$$

$$s0 = ld' \cdot shr' \cdot shl + ld$$

# Register Operation Table

Inputs			Outputs		Note		Inputs				Outputs		Note
ld	shr	shl	s1	s0	Operation		ld	shr	shl		s1	s0	Operation
0	0	0	0	0	Maintain value	→	0	0	0		0	0	Maintain value
0	0	1	1	1	Shift left	→	0	0	1		1	1	Shift left
0	1	0	1	0	Shift right	→	0	1	X		1	0	Shift right
0	1	1	1	0	Shift right	→	1	X	X		1	0	Parallel load
1	0	0	0	1	Parallel load	→					0	1	Parallel load
1	0	1	0	1	Parallel load	→					0	1	Parallel load
1	1	0	0	1	Parallel load	→					0	1	Parallel load
1	1	1	0	1	Parallel load	→					0	1	Parallel load

- Register operations are typically shown using compact version of table
  - X means same operation whether the value is 0 or 1
    - One X expands to two rows
    - Two Xs expand to four rows
  - Put the highest priority control input on the left to make the reduced table simpler

# Register Design Process

**Four-step process for designing a multifunction register.**

Step	Description
1. <i>Determine mux size</i>	Count the number of operations (don't forget the maintain present value operation!) and add in front of each flip-flop a mux with at least that number of inputs.
2. <i>Create mux operation table</i>	Create an operation table defining the desired operation for each possible value of the mux select lines.
3. <i>Connect mux inputs</i>	For each operation, connect the corresponding mux data input to the appropriate external input or flip-flop output (possibly passing through some logic) to achieve the desired operation.
4. <i>Map control lines</i>	Create a truth table that maps external control lines to the internal mux select lines, with appropriate priorities, and then design the logic to achieve that mapping

# Register Design Example (1/2)

- Desired register operations
  - Load, shift left, synchronous clear, synchronous set

## Step 1: Determine mux size

5 operations (with maintain present value, don't forget this one!) --> **Use 8x1 mux**

## Step 2: Create mux operation table

## Step 3: Connect mux inputs


## Step 4: Map control lines

$$s2 = \text{clr}' * \text{set}$$

$$s1 = \text{clr}' * \text{set}' * \text{ld}' * \text{shl} + \text{clr}$$


$$s0 = \text{clr}' * \text{set}' * \text{ld} + \text{clr}$$

s2	s1	s0	Operation
0	0	0	Maintain present value
0	0	1	Parallel load
0	1	0	Shift left
0	1	1	Synchronous clear
1	0	0	Synchronous set
1	0	1	Maintain present value
1	1	0	Maintain present value
1	1	1	Maintain present value

 

Inputs				Outputs			Operation
clr	set	ld	shl	s2	s1	s0	
0	0	0	0	0	0	0	Maintain present value
0	0	0	1	0	1	0	Shift left
0	0	1	X	0	0	1	Parallel load
0	1	X	X	1	0	0	Set to all 1s
1	X	X	X	0	1	1	Clear to all 0s

# Register Design Example (2/2)

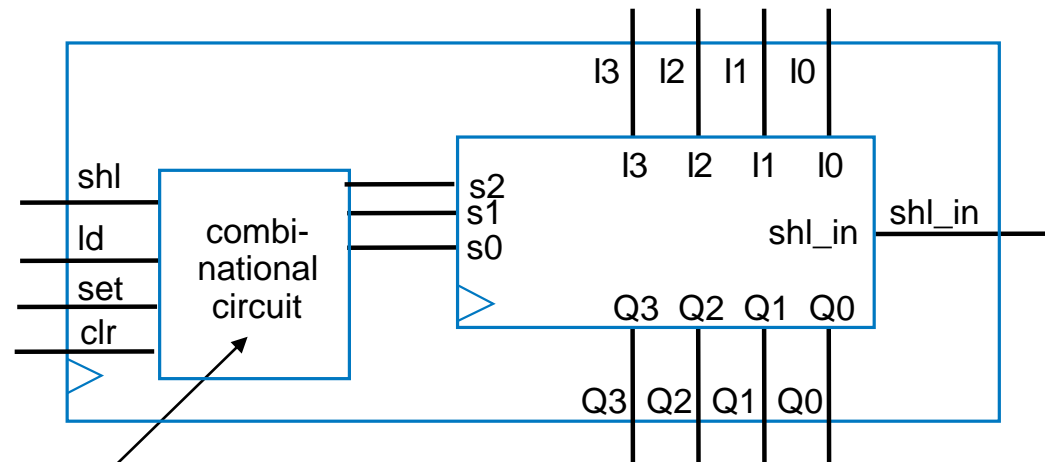

## Step 4: Map control lines

$$s2 = \text{clr}' * \text{set}$$

$$s1 = \text{clr}' * \text{set}' * \text{ld}' * \text{shl} + \text{clr}$$

$$s0 = \text{clr}' * \text{set}' * \text{ld} + \text{clr}$$

Inputs				Outputs			Operation
clr	set	ld	shl	s2	s1	s0	
0	0	0	0	0	0	0	Maintain present value
0	0	0	1	0	1	0	Shift left
0	0	1	X	0	0	1	Parallel load
0	1	X	X	1	0	0	Set to all 1s
1	X	X	X	0	1	1	Clear to all 0s