

B38DB: Digital Design and Programming

Sequential Logic Design – Finite State Machines


Mustafa Suphi Erden

Heriot-Watt University
School of Engineering & Physical Sciences
Electrical, Electronic and Computer Engineering
Room: EM 2.01
Phone: 0131-4514159
E-mail: m.s.erden@hw.ac.uk


Reminder: Bit Storage Summary

We designed a new building block, a **flip-flop**, that stores one bit.


What will we do with this?

 

 
Feature: $S=1$ sets Q to 1, $R=1$ resets Q to 0.
Problem: $SR=11$ yield undefined Q .



 Feature: S and R only have effect when $C=1$. We can design outside circuit so $SR=11$ never happens when $C=1$.
Problem: avoiding $SR=11$ can be a burden.



 Feature: SR can't be 11 if D is stable before and while $C=1$, and will be 11 for only a brief glitch even if D changes while $C=1$.
Problem: $C=1$ too long propagates new values through too many latches: too short may not enable a store.





Feature: Only loads D value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle. Tradeoff: uses more gates internally than D latch, and requires more external gates than SR – but gate count is less of an issue today.

Introduction

- We will:
 - Combine flip-flops to build a multi-bit storage **register**
 - Describe the sequential behavior using a **finite state machine (FSM)**
 - Convert a FSM to a **controller** – a sequential circuit having a register and combinational logic


Register

  - Typically, we store multi-bit items
 - e.g., storing a 4-bit binary number
- Register**: multiple flip-flops sharing a clock signal



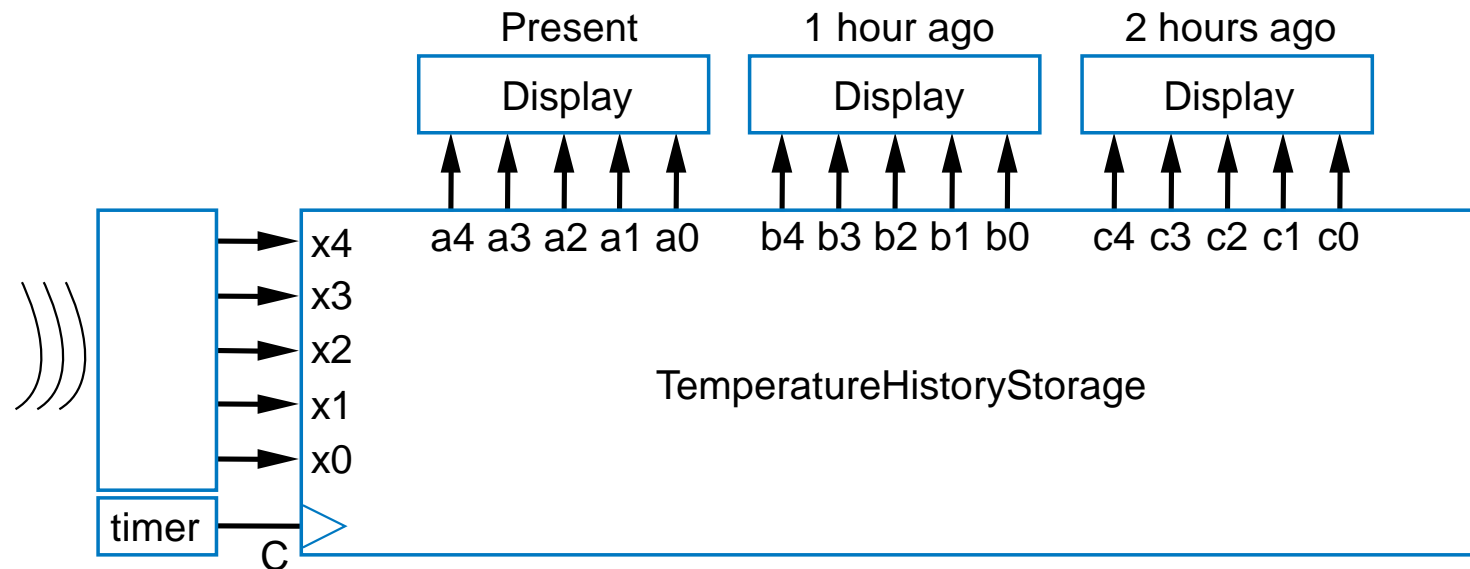Example Using Registers: Temperature Display (1/2)


- Temperature history display
 - Sensor outputs temperature as 5-bit binary number
 - Timer pulses C every hour
 - Record temperature on each pulse, display the last three recorded values



(In practice, we would actually avoid connecting the timer output C to a clock input, instead we would connect only an oscillator output to a clock input.)



Example Using Registers: Temperature Display (2/2)

- Use three 5-bit registers

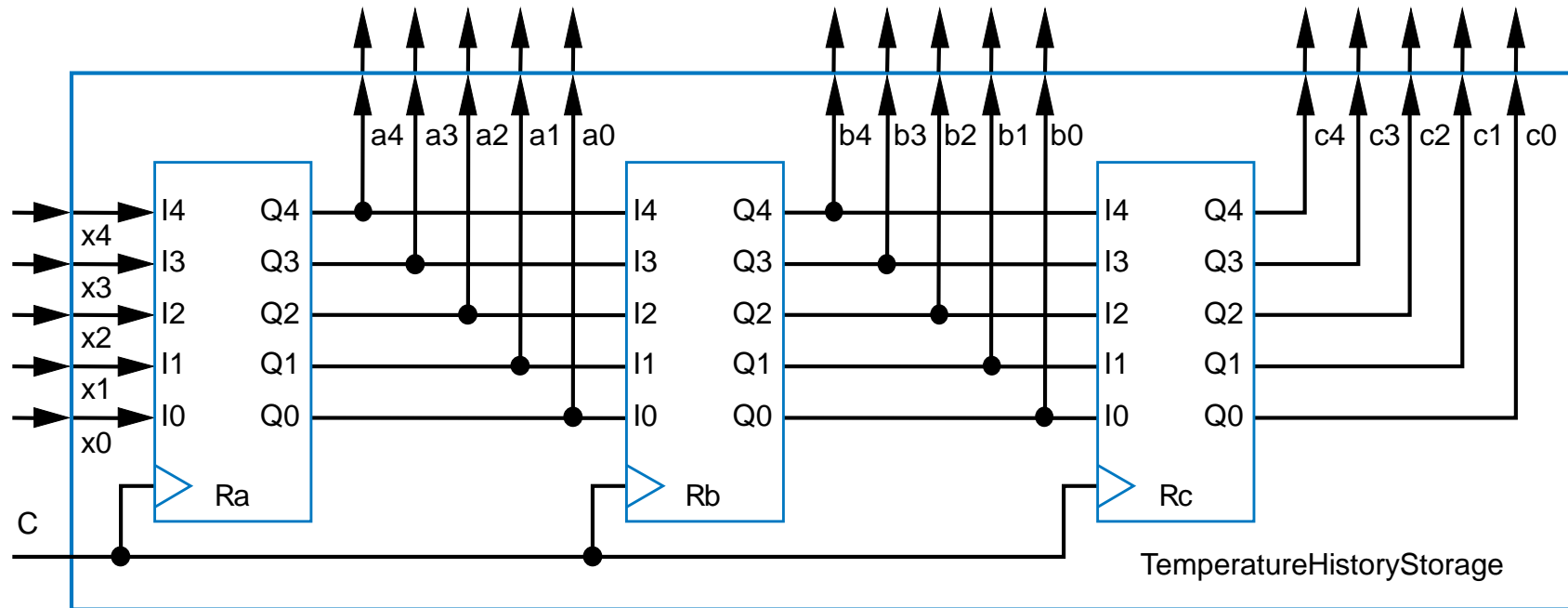

Finite-State Machines (FSMs) and Controllers

 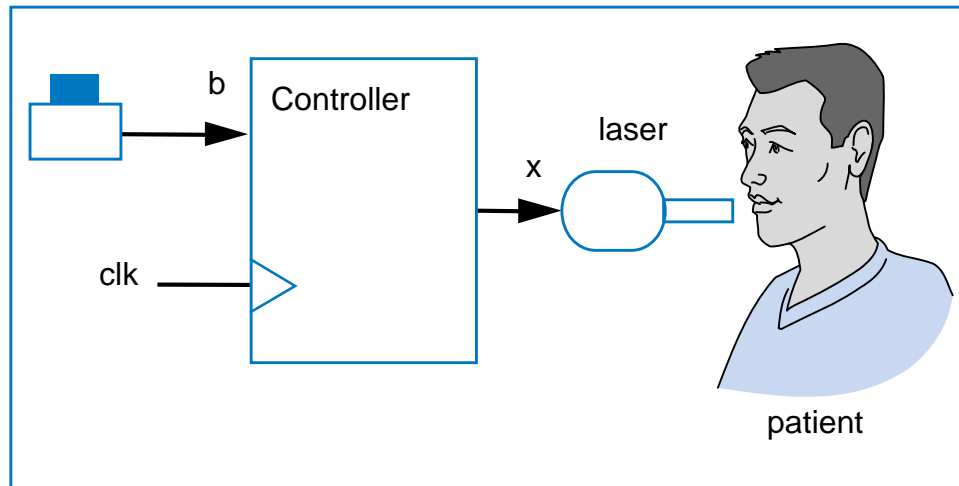- We want to have sequential circuits with particular behavior over time
- Example: Laser timer
 - Push button: $x=1$ for 3 clock cycles



How to Design Sequential Circuits

- **Combinational circuit** design process had two important things:
 1. A formal way to describe desired circuit behavior
 - Boolean equation, or truth table
 2. A well-defined process to convert that behavior into a circuit
 - Using Karnaugh maps



- We need similar methods for **sequential circuit design**:
 1. How to describe desired behavior?
 - **Finite State Machines**
 2. How to convert that behavior into a circuit?
 - **Controller**

FSM: Describing Behavior of a Sequential Circuit

■ Finite-State Machine (FSM)

- Define **states** and **transitions** among the states
 - Example:
 - Make x change its toggle (0 to 1 and 1 to 0) every clock cycle
 - Two states: “Off” ($x=0$), and “On” ($x=1$)
 - Arrow with no starting state points to the initial state (when the circuit first starts)



Output: x

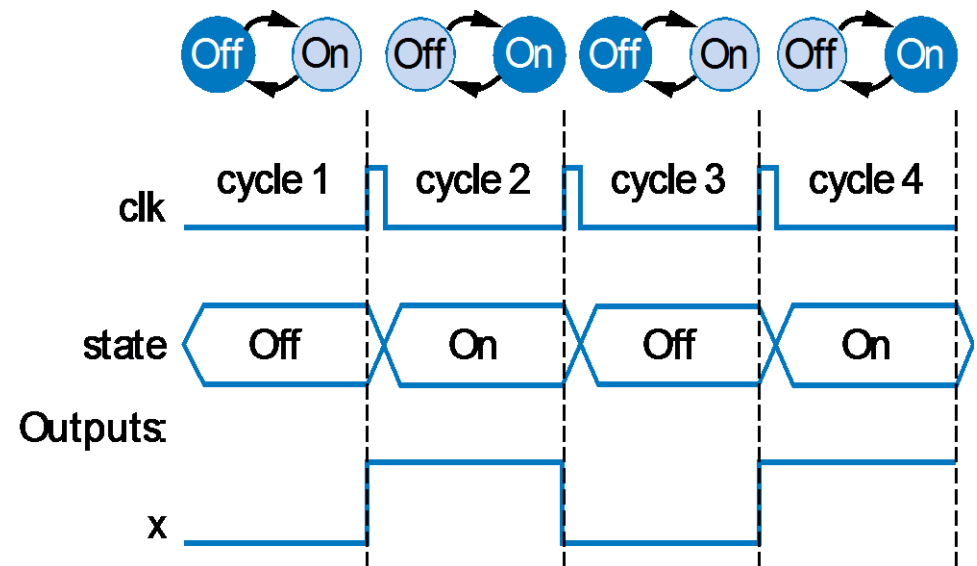 

FSM Example: 0,1,1,1, repeating

- We want to generate the 0, 1, 1, 1, 0, 1, 1, 1, ... sequence
 - Each value is for one clock cycle
- Describe it as a FSM
 - Four states
 - Transition on rising clock edge to the next state



Outputs: x

  

FSM for Three-Cycles High Laser Timer



- Four states
- Wait in the “Off” state while b is 0 (b')
- When b is 1 (and rising clock edge), transition to On1
 - Sets $x=1$
 - On the next two clock edges, transition to On2, then to On3, which also set $x=1$
- So $x=1$ for three cycles after the button is pressed

Input: b ; Output: x

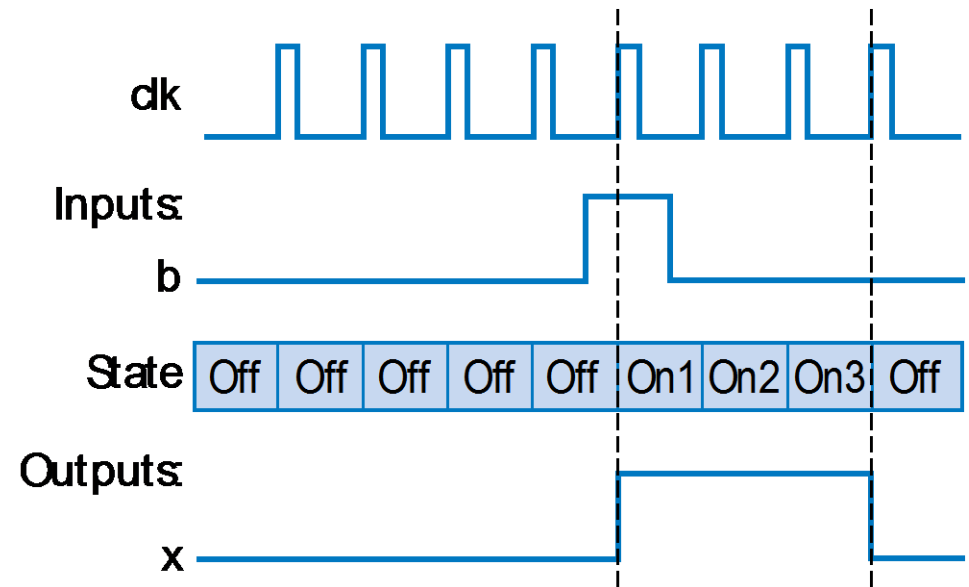 

FSM Simplification: Rising Clock Edges Implicit

 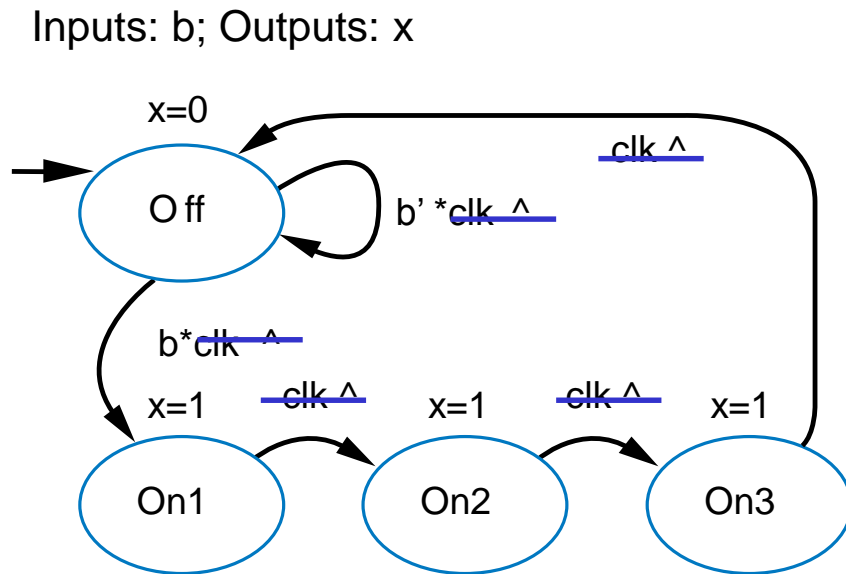
- Assume every edge has a rising clock, even if not shown
 - In this course: Only consider **synchronous** FSMs:
rising edge on every transition



Note: the transitions with no associated condition show direct transitions to the next state on the next clock cycle

FSM Definition

 - FSM consists of
 - Set of **states**
 - Ex: $\{Off, On1, On2, On3\}$
 - Set of **inputs**, set of **outputs**
 - Ex: Inputs: $\{b\}$, Outputs: $\{x\}$
 - **Initial state**
 - Ex: “*Off*”
 - Set of **transitions**
 - Describe the next states
 - Ex: *Has 5 transitions*
 - Set of **actions**
 - Sets outputs while in the states
 - Ex: $x=0$, $x=1$, $x=1$, and $x=1$




We often draw FSM graphically, known as a **state diagram**

We can also use a table (state table), or textual languages

FSM Example: Code Detector

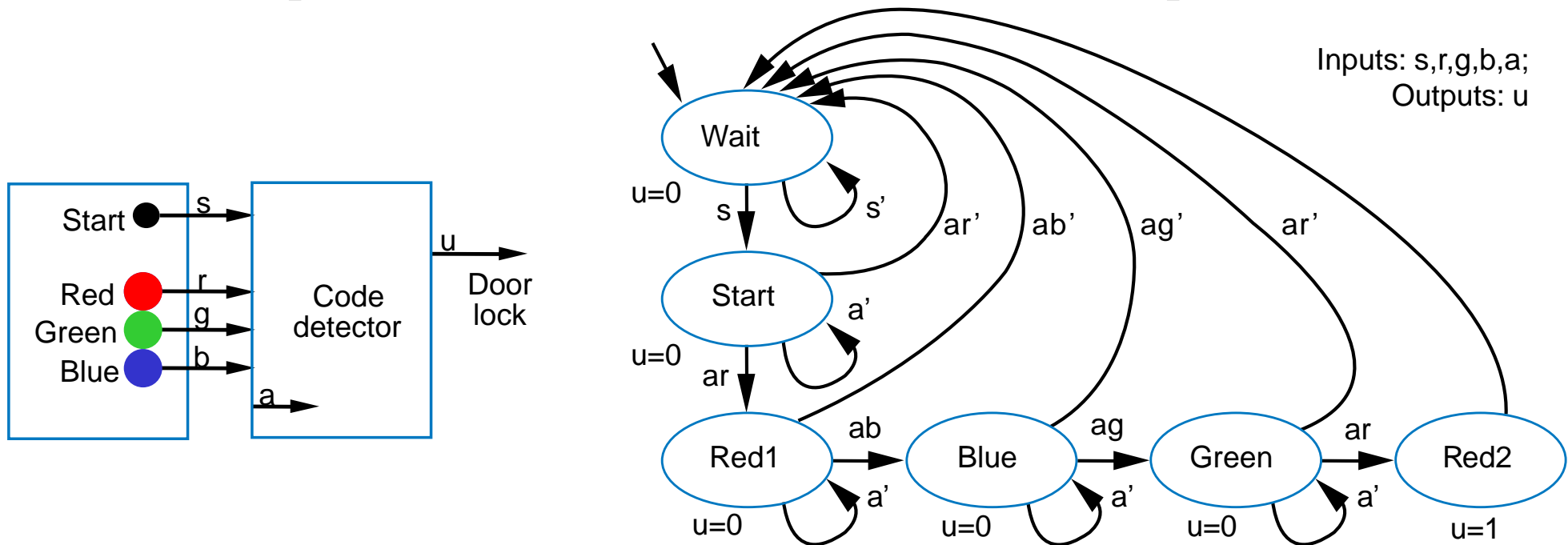
- Unlock the door ($u=1$) only when the buttons are pressed in correct order:
 - **start, red, blue, green, red**
- Input from each button: s, r, g, b
 - Also, input a indicates that some colored button is pressed



Q: Can you trick this FSM to open the door, without knowing the code?

A: Yes, hold all buttons simultaneously

Improve FSM for Code Detector

 

- New transition conditions detect when wrong button is pressed, and returns to “Wait”
- Still something is wrong with this FSM, but we will discover it next week.