

B38EM Introduction to Electricity and Magnetism Lecture 10

Transmission Lines

Dr. Yuan Ding (Heriot-Watt University)
yuan.ding@hw.ac.uk
yding04.wordpress.com

Outline & Outcome

- Lumped or distributed?
- Transmission line theory
- Terminated transmission line
- Smith Chart


References & Resources

- Elements of Electromagnetics (7th Edition), by Sadiku, Oxford University Press
- Fundamentals of Applied Electromagnetics (7th Edition), by Ulaby and Ravaioli
- Field and Wave Electromagnetics (2nd Edition), by David Cheng


Transmission Lines

Common Types


(TEM waves)

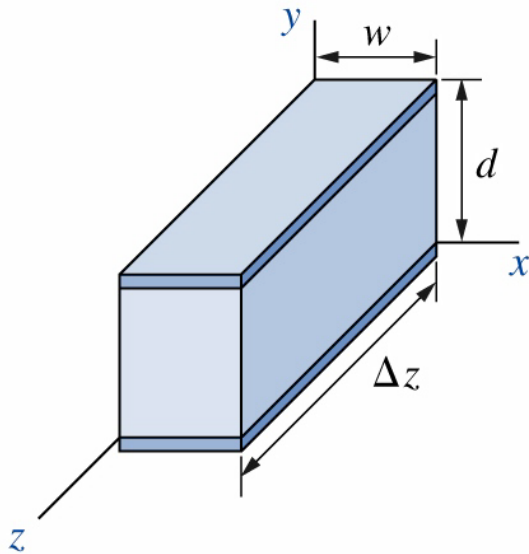

Parallel-plate
transmission line

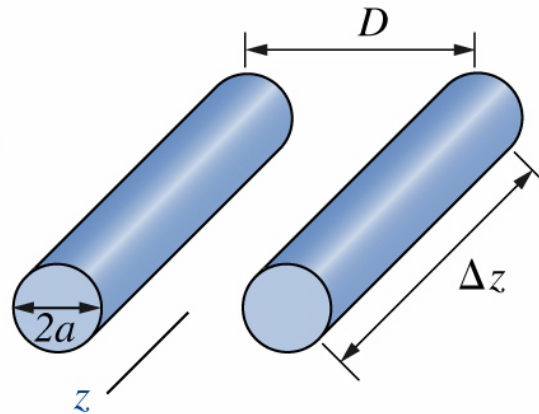

Two-wire (twin-lead)
transmission line

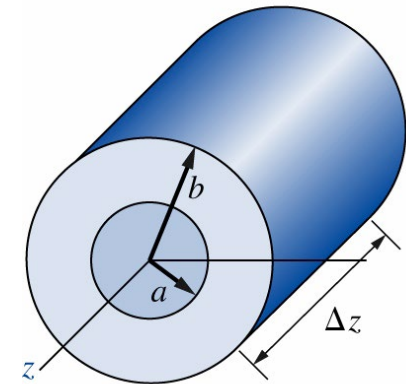

Coaxial
transmission line


Each structure (including the twin lead) may have a dielectric between two conductors used to keep the separation between the metallic elements constant, so that the electrical properties would be constant.

Transmission Lines

Common Types

(TEM waves)




Microstrip line

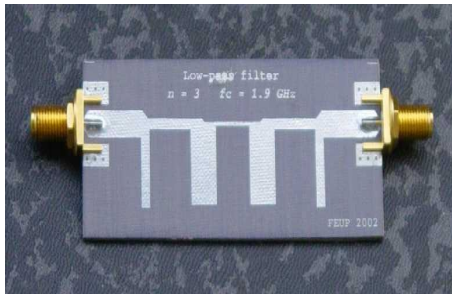

Twin lead



Coaxial cable

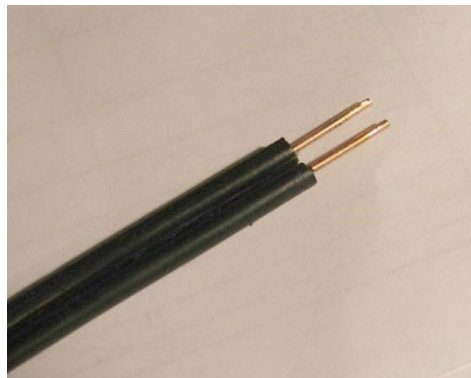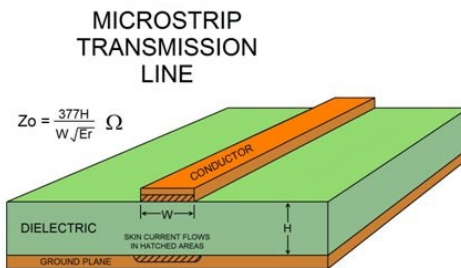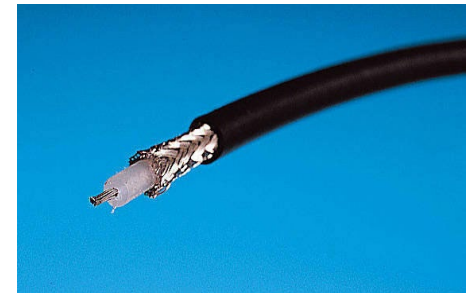


Transmission Lines

Lumped or Distributed?

Example: Inductor

Low-frequency


(lumped)

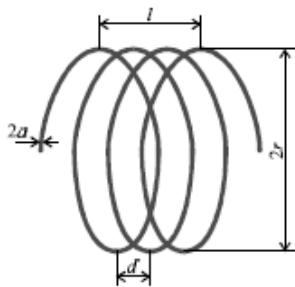

$$Z = R + j\omega L$$



High-frequency

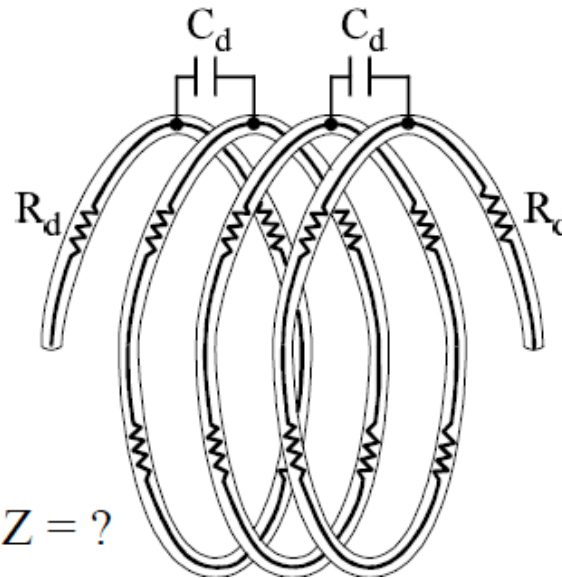

$$Z = ?$$

Transmission Lines

Lumped or Distributed?

At low frequencies:

Can simply use a wire to connect two components


$$f = 50 \text{ Hz}, \quad \text{wavelength} = 6 \times 10^6 \text{ m};$$

At high frequencies:

Cannot simply use a wire to connect two components

$$f = 500 \text{ MHz}, \quad \text{wavelength} = 0.6 \text{ m};$$

Transmission Lines

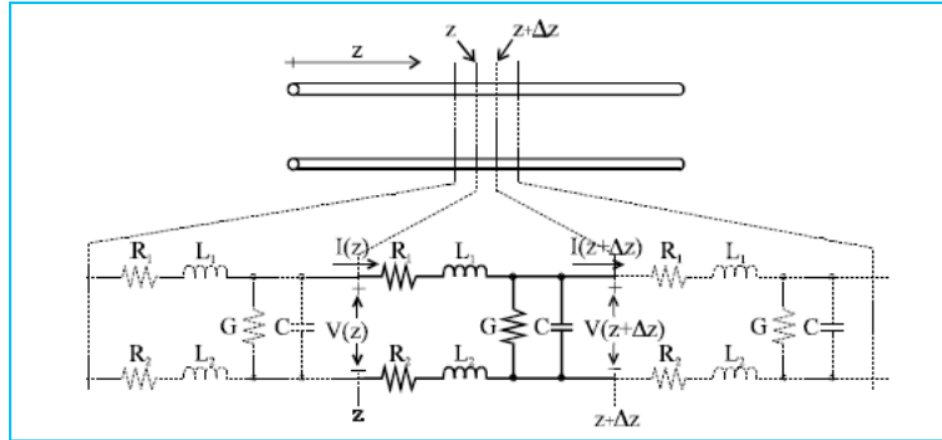

- R = series resistance per unit length, for both conductors, in Ω/m ;
- L = series inductance per unit length, for both conductors, in H/m ;
- G = parallel conductance per unit length, in S/m ;
- C = parallel capacitance per unit length, in F/m .
- **Loss:** R (due to the finite conductivity) + G (due to the dielectric loss)

Transmission Lines

Transmission line theory


- Bridges the gap between field analysis and basic circuit theory
- Extension from lumped to distributed theory
- A specialization of Maxwell's equations
- Significant importance in microwave network analysis

The key difference between circuit theory and transmission line theory is electrical size. Circuit analysis assumes that the physical dimensions of a network are much smaller than the electrical wavelength, while transmission lines may be a considerable fraction of a wavelength, or many wavelengths, in size. Thus a transmission line is a **distributed-parameter network**, where voltages and currents can vary in magnitude and phase over its length.

Transmission Lines

Parallel-plate transmission line

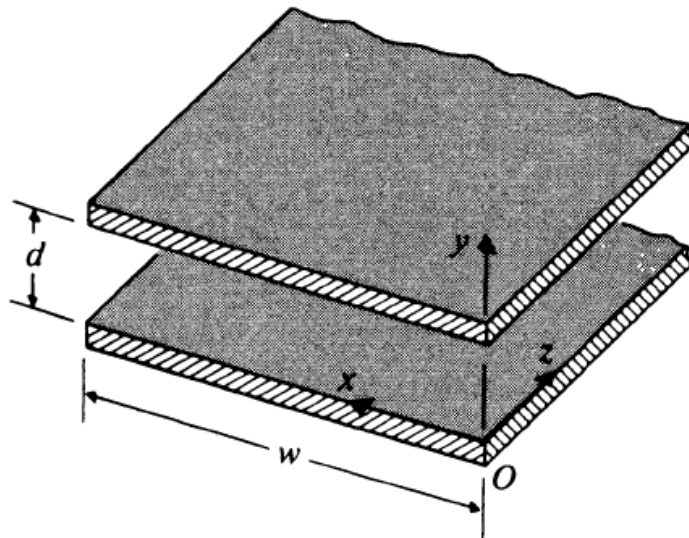From Maxwell's equations to Transmission line equation



$$\nabla^2 \mathbf{E} - \frac{1}{c^2} \frac{\partial^2 \mathbf{E}}{\partial t^2} = 0 \quad \text{since } \mathbf{E} \propto e^{i\omega t} \rightarrow \nabla^2 \mathbf{E} + \frac{\omega^2}{c^2} \mathbf{E} = 0 \quad (\nabla^2 \mathbf{E} + k_0^2 \mathbf{E} = 0)$$

Transmission Lines



Parallel-plate transmission line

$$\nabla^2 \mathbf{E} - \frac{1}{c^2} \frac{\partial^2 \mathbf{E}}{\partial t^2} = 0 \quad \text{since } \mathbf{E} \propto e^{i\omega t} \rightarrow \nabla^2 \mathbf{E} + \frac{\omega^2}{c^2} \mathbf{E} = 0 \quad (\nabla^2 \mathbf{E} + k_0^2 \mathbf{E} = 0)$$

Assume it's a plane wave propagate in the z -axis with polarization in the y -axis direction.

$$\frac{d^2}{dz^2} E_y + k_0^2 E_y = 0 \rightarrow \mathbf{E} = \hat{y} \tilde{E}_0 e^{-ik_0 z + i\omega t}$$
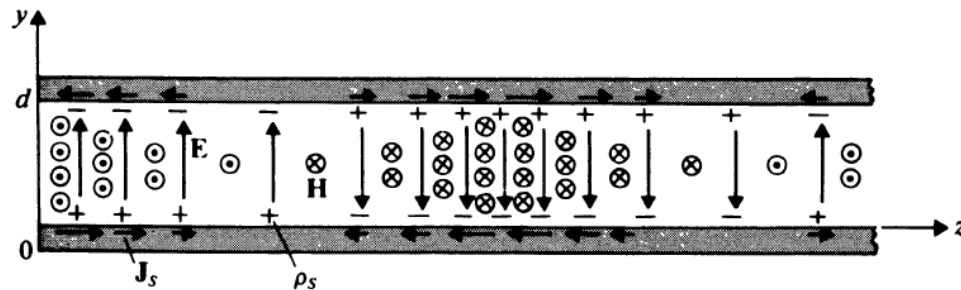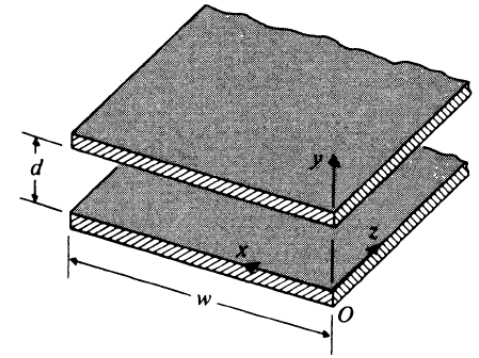
$$\mathbf{H} = -\hat{x} \frac{1}{\sqrt{\frac{\mu}{\epsilon}}} \tilde{E}_0 e^{-ik_0 z + i\omega t} = H_x \hat{x}$$



Transmission Lines



Parallel-plate transmission line

Crossing the boundary from dielectric medium to the perfect conduction plates:

$$\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t} \quad \& \quad \nabla \times \vec{B} = \mu\epsilon \frac{\partial \vec{E}}{\partial t}$$

$$\rightarrow \nabla \times \vec{E} = -i\omega\mu\vec{H} \quad \& \quad \nabla \times \vec{H} = i\omega\epsilon\vec{E}$$
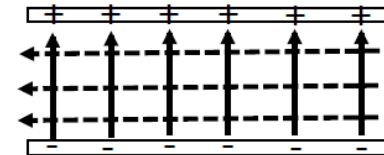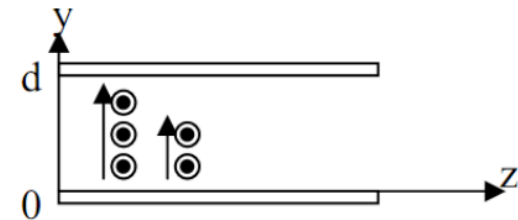
$$\mathbf{E} = \hat{y}\tilde{E}_y(z,t), \quad \mathbf{H} = \hat{x}\tilde{H}_x(z,t) \quad (\vec{E} \rightarrow V, \vec{H} \rightarrow \sigma \rightarrow I)$$



Basic differential equations

$$\begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ 0 & E_y & 0 \end{vmatrix} = -i\omega\mu H_x \rightarrow \frac{dE_y}{dz} = i\omega\mu H_x \quad \& \quad \frac{dH_x}{dz} = i\omega\epsilon E_y$$

Transmission Lines



Parallel-plate transmission line

$$\int_0^d \frac{dE_y}{dz} dy = i\omega\mu \int_0^d H_x dy \quad \rightarrow \quad -\frac{dV(z)}{dz} = i\omega LI(z)$$

$L = \mu \frac{d}{w}$ is the inductance per unit length

$$\int_0^w \frac{dH_x}{dz} dx = i\omega\varepsilon \int_0^w E_y dx \quad \rightarrow \quad -\frac{dI(z)}{dz} = i\omega CV(z)$$

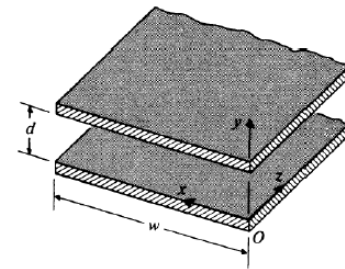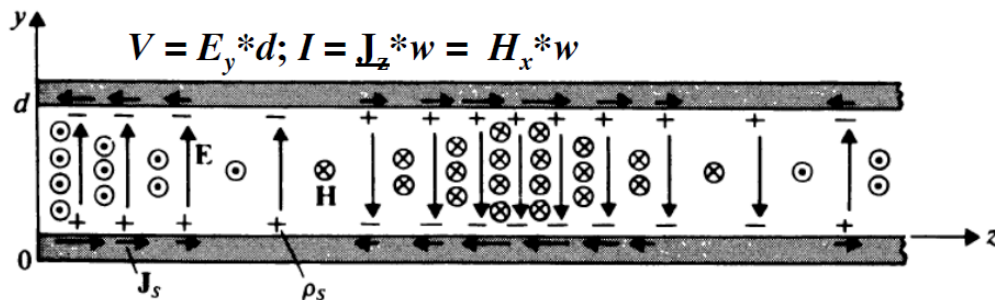$C = \varepsilon \frac{w}{d}$ is the capacitance per unit length



Transmission Lines

Time-harmonic transmission line equations

$$\begin{array}{lcl}
 -\frac{dV(z)}{dz} = i\omega LI(z) & \left. \begin{array}{c} \\ \\ \end{array} \right\} & \frac{d^2V(z)}{dz^2} = -\omega^2 LC V(z) \quad \longrightarrow \quad V(z) = V_0 e^{-ikz} \\
 -\frac{dI(z)}{dz} = i\omega CV(z) & & \frac{d^2I(z)}{dz^2} = -\omega^2 LC I(z) \quad \longrightarrow \quad I(z) = I_0 e^{-ikz}
 \end{array}$$

$(k = \omega\sqrt{LC})$


Characteristic impedance:
$$Z_0 = \frac{V(z)}{I(z)} = \frac{V_0}{I_0} = \frac{\omega LI_0}{kI_0} = \sqrt{\frac{L}{C}} = \sqrt{\frac{\mu d / w}{\epsilon w / d}} = \frac{d}{w} \sqrt{\frac{\mu}{\epsilon}}$$

Phase velocity :
$$v = \frac{\omega}{k} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(\mu d / w)(\epsilon w / d)}} = \frac{1}{\sqrt{\mu \epsilon}}$$

$L = \mu \frac{d}{w}$ $C = \epsilon \frac{w}{d}$

Transmission Lines

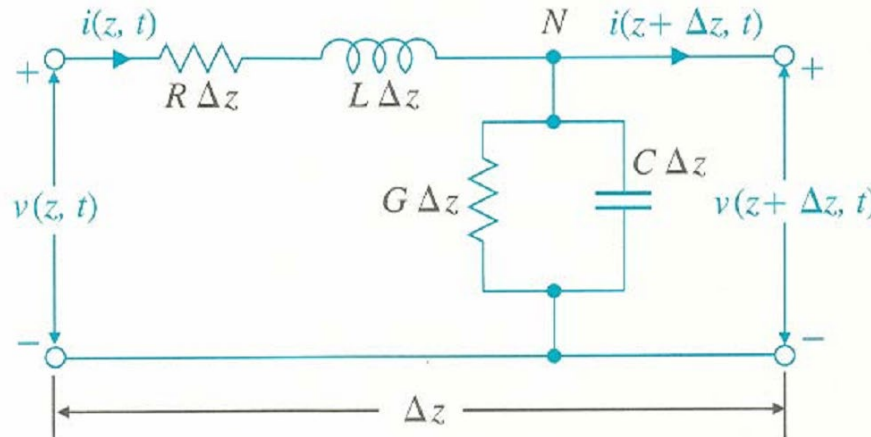Time-harmonic transmission line equations



$$-\frac{dV(z)}{dz} = (R + i\omega L)I(z)$$

$$-\frac{dI(z)}{dz} = (G + i\omega C)V(z)$$



$$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$$

$$\frac{d^2 I(z)}{dz^2} = \gamma^2 I(z),$$

Where $\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (m^{-1})$

α : attenuation constant

β : phase constant

Transmission Lines

Time-harmonic transmission line equations

$$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$$



$$V(z) = V^+(z) + V^-(z) \\ = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z},$$

Wave propagation in the
positive z direction

$$\frac{d^2 I(z)}{dz^2} = \gamma^2 I(z),$$



$$I(z) = I^+(z) + I^-(z) \\ = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z},$$

Wave propagation in the
negative -z direction



$$\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \frac{R + j\omega L}{\gamma}$$

Characteristic impedance:

$$Z_0 = \frac{R + j\omega L}{\gamma} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (\Omega)$$

Transmission Lines

Time-harmonic transmission line equations

Lossless Line ($R = 0, G = 0$).

a) Propagation constant:

$$\begin{aligned}\gamma &= \alpha + j\beta = j\omega\sqrt{LC}; \\ \alpha &= 0, \\ \beta &= \omega\sqrt{LC} \quad (\text{a linear function of } \omega).\end{aligned}$$

b) Phase velocity:

$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad (\text{constant}).$$

c) Characteristic impedance:


$$\begin{aligned}Z_0 &= R_0 + jX_0 = \sqrt{\frac{L}{C}}; \\ R_0 &= \sqrt{\frac{L}{C}} \quad (\text{constant}), \\ X_0 &= 0.\end{aligned}$$

Transmission Lines

Terminated transmission line

Lossless: $\alpha=0$; $\gamma=j\beta$

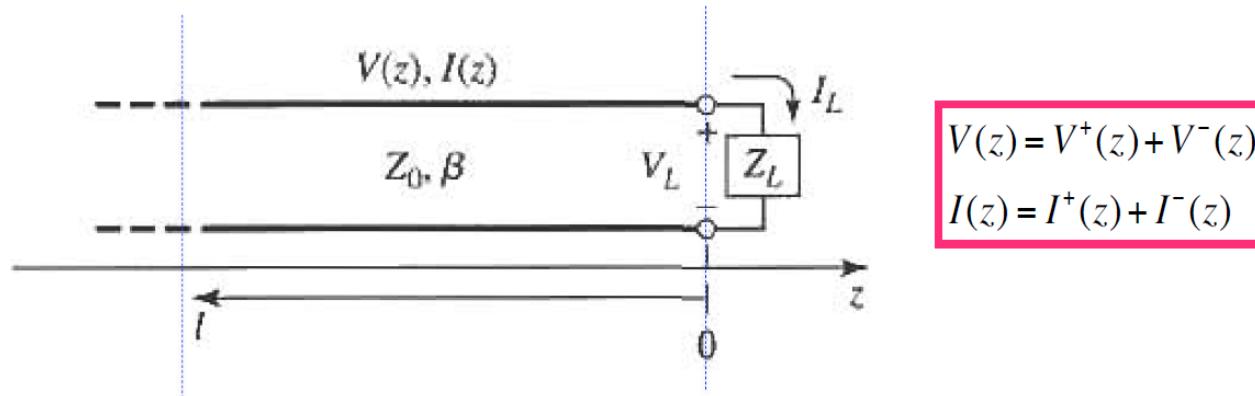What is a voltage reflection coefficient?



- Assume an incident wave ($V_0^+ e^{-j\beta z}$) generated from a source at $z < 0$. We have seen that the ratio of voltage to current for such a traveling wave is Z_0 , the characteristic impedance. But when the line is terminated in an arbitrary load $Z_L \neq Z_0$, the ratio of voltage to current at the load must be Z_L . Thus, a reflected wave must be excited with the appropriate amplitude to satisfy this condition.

Transmission Lines


Terminated transmission line

Lossless: $\alpha=0$; $\gamma=j\beta$

Total voltage and current on the line
(superposition of incident and reflected waves):

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$
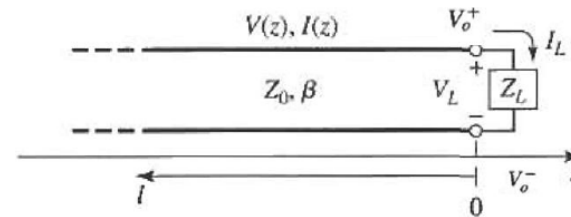
$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$



(V_0^+ : incident voltage at $z=0$; V_0^- : reflected voltage at $z=0$)

The total voltage and current at the load are related by the load impedance, so at $z=0$, we must have

$$Z_L = \frac{V(0)}{I(0)} = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} Z_0$$

Voltage reflection coefficient Γ_0 :

$$\Gamma_0 = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_0 = 0 \quad (Z_L = Z_0)$$

$$\Gamma_0 = 1 \quad (Z_L \rightarrow \infty)$$

$$\Gamma_0 = -1 \quad (Z_L \rightarrow 0)$$

(Phase difference: π)

Transmission Lines


Terminated transmission line

Lossless: $\alpha=0$; $\gamma=j\beta$

The total voltage and current waves on the line :

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} = V_0^+ [e^{-j\beta z} + \Gamma_0 e^{j\beta z}]$$
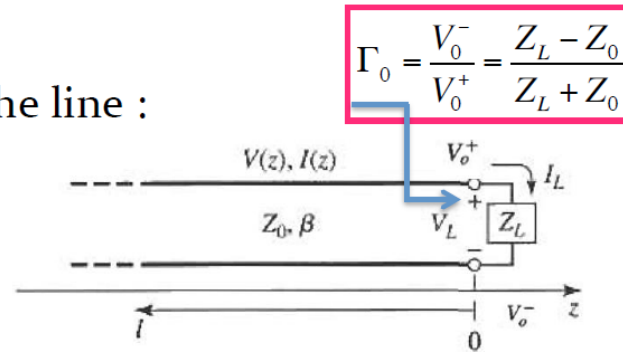
$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z} = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_0 e^{j\beta z}]$$



Consider the time-average power flow along the line at the point z :

$$P_{av} = \frac{1}{2} \text{Re}[V(z)I(z)^*] = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \text{Re}\{1 - \Gamma_0^* e^{-2j\beta z} + \Gamma_0 e^{2j\beta z} - |\Gamma_0|^2\}$$

which can be simplified:


$$P_{av} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma_0|^2)$$

- **Constant average power flow at any point on the line;**
- **Total power delivered to the load = incident power – reflected power**


Transmission Lines

Terminated transmission line

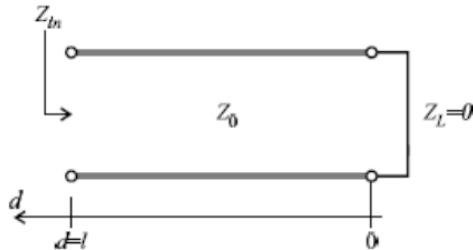(a). Standing wave ($\Gamma_0 = -1$) $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} = V_0^+ [e^{-j\beta z} + \Gamma_0 e^{j\beta z}]$


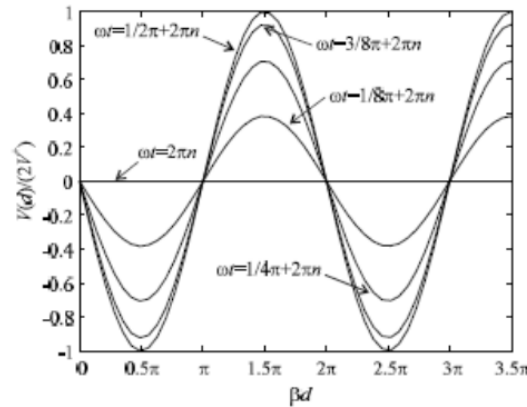
$$v(d, t) = 2V^+ \sin(\beta d) \cos(\omega t + \pi/2)$$



(b). Voltage standing wave ratio ($|\Gamma_0| < 1$)

$$|V(z)| = |V_0^+| |1 + \Gamma_0 e^{2j\beta z}| = |V_0^+| |1 + \Gamma_0 e^{-2j\beta l}| \quad (z = -l)$$

$$SWR = \frac{|V|_{\max}}{|V|_{\min}} = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|} \quad (1 \leq SWR < \infty, \text{ where } SWR=1 \text{ implied a match load.})$$

$$RL = -20 \log |\Gamma_0| \quad (dB) \quad (\text{return loss})$$

Transmission Lines


Terminated transmission line

Reflection coefficient at $z = -l$ and input impedance Z_{in}

Reflection coefficient Γ_l at $z = -l$:

$$\Gamma_l = \frac{V^-(z)}{V^+(z)} \Big|_{z=-l} = \frac{V_0^- e^{j\beta^*(-l)}}{V_0^+ e^{-j\beta^*(-l)}} = \frac{V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l}} = \Gamma_0 e^{-2j\beta l}$$
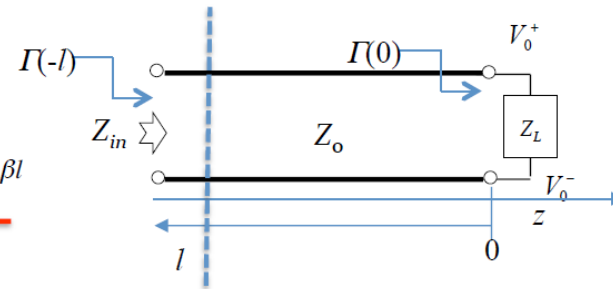
$$[V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}, \quad \Gamma_0 = \frac{V_0^-}{V_0^+}]$$



At a distance l from the load, **the input impedance Z_{in}** seen looking toward the load is

$$\begin{aligned} Z_{in} &= \frac{V(-l)}{I(-l)} = \frac{V_0^+ (e^{j\beta l} + \Gamma_0 e^{-j\beta l})}{V_0^+ (e^{j\beta l} - \Gamma_0 e^{-j\beta l})} Z_0 \\ &= \frac{1 + \Gamma_0 e^{-2j\beta l}}{1 - \Gamma_0 e^{-2j\beta l}} Z_0 \\ &= \frac{1 + \Gamma_l}{1 - \Gamma_l} Z_0 \end{aligned}$$

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_0 e^{j\beta z}]$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_0 e^{j\beta z}]$$

$$\Gamma_l = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

Transmission Lines

Terminated transmission line

Reflection coefficient at $z = -l$ and input impedance Z_{in}

A more usable form of input impedance:


$$Z_{in} = \frac{1 + \Gamma_0 e^{-2j\beta l}}{1 - \Gamma_0 e^{-2j\beta l}} Z_0 \quad \boxed{\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0}}$$

$$= Z_0 \frac{(Z_L + Z_0)e^{j\beta l} + (Z_L - Z_0)e^{-j\beta l}}{(Z_L + Z_0)e^{j\beta l} - (Z_L - Z_0)e^{-j\beta l}}$$

$$= Z_0 \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l}$$

$$= \boxed{Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}}$$

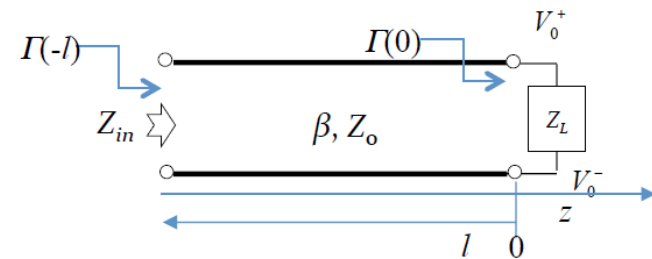• Input impedance of a portion of transmission line with an arbitrary load impedance.




$$\boxed{\Gamma_l = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}}$$

Transmission Lines

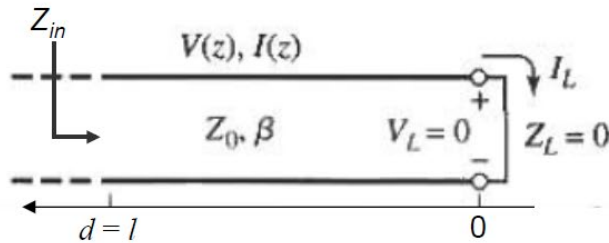(1). Short-circuit transmission line ($Z_L=0$, $\Gamma_0=-1$)

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_0 e^{j\beta z}]$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_0 e^{j\beta z}]$$



Voltage:

$$V(d) = 2jV^+ \sin(\beta d)$$


Current:

$$I(d) = \frac{2V^+}{Z_0} \cos(\beta d)$$


Impedance

$$Z_{in}(d) = jZ_0 \tan(\beta d)$$


Imaginary
number

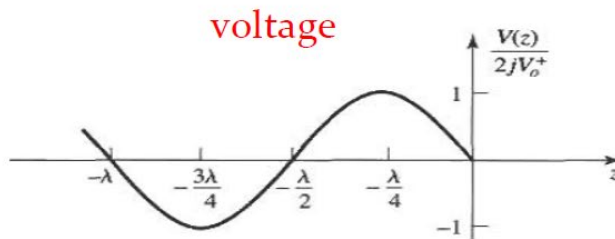

(a)

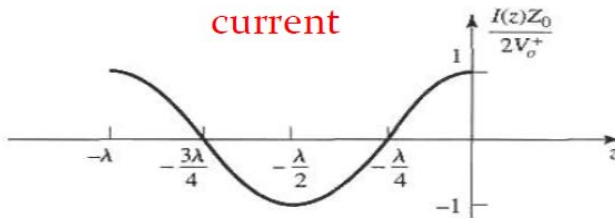

(b)

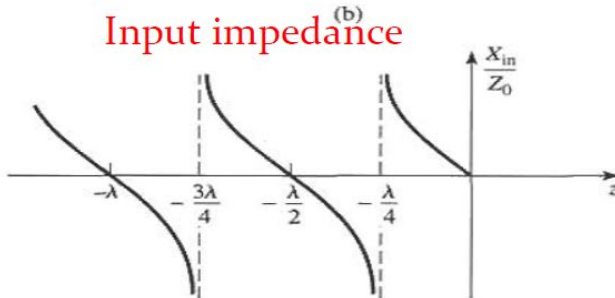


(c)

Transmission Lines

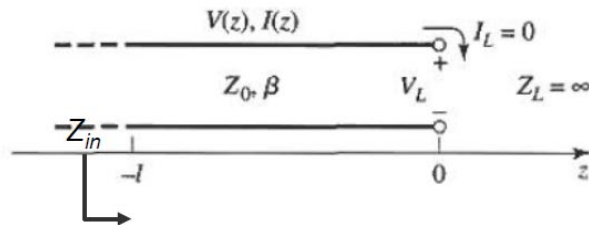(2). Open-circuit transmission line ($Z_L = \infty$, $\Gamma_0 = 1$)

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_0 e^{j\beta z}]$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_0 e^{j\beta z}]$$



Voltage:

$$V(d) = 2V^+ \cos(\beta d)$$


Current:

$$I(d) = \frac{2jV^+}{Z_0} \sin(\beta d)$$


Impedance

$$Z_{in}(d) = -jZ_0 \cot(\beta d)$$


Imaginary
number

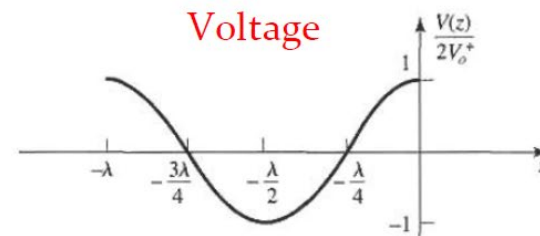

(a)

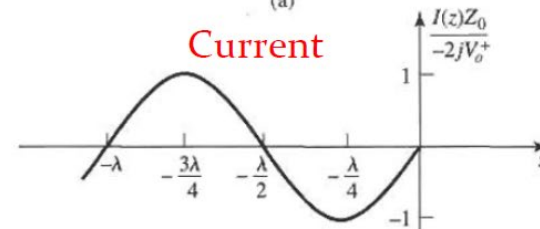

(b)


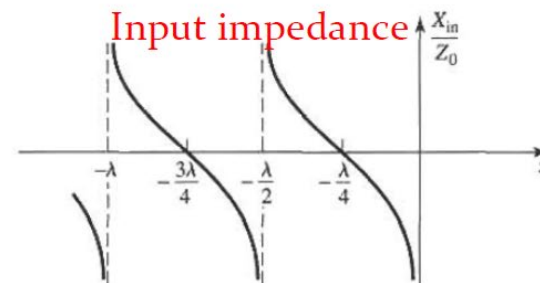


(c)

Transmission Lines

Q: Find the position l to place an impedance element Z' ($Z'=Z_0$) so that Γ is zero in the case of $Z_L = 0$ or infinite.

(1) $Z_L = 0$

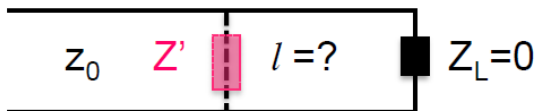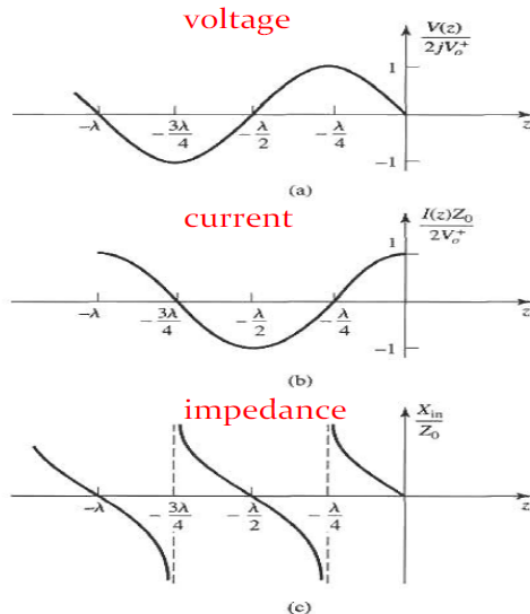

$$\Gamma_l = \frac{Z_{in}(l) - Z_0}{Z_{in}(l) + Z_0} = 0$$


$$Z_{in}(l) = Z_0$$

$$Z'_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

$$\frac{1}{Z_{in}(l)} = \frac{1}{Z'_{in}} + \frac{1}{Z'}$$


$$Z'_{in} \rightarrow \infty \text{ \& } l = (2m+1) * \lambda/4$$

$$m=0, 1, 2, 3, \dots$$

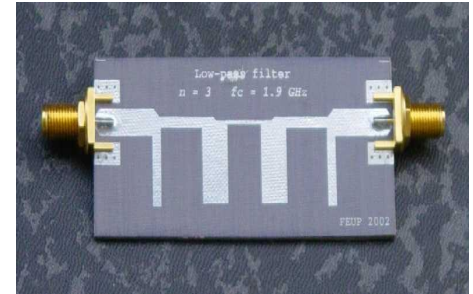

Transmission Lines

(3). Quarter-wave transmission line

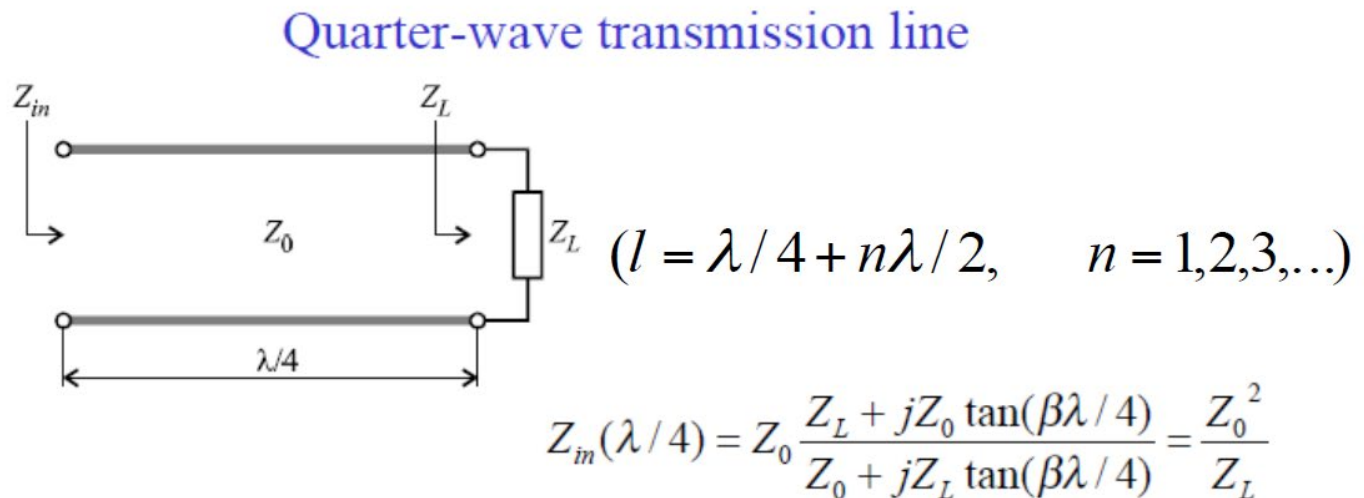

Quarter-wave transformer model:
given input and output impedances

Predict line
impedance


$$Z_0 = \sqrt{Z_L Z_{in}}$$

Smith Chart: Introduction

Introduction

A graphical tool used to solve transmission line problems.

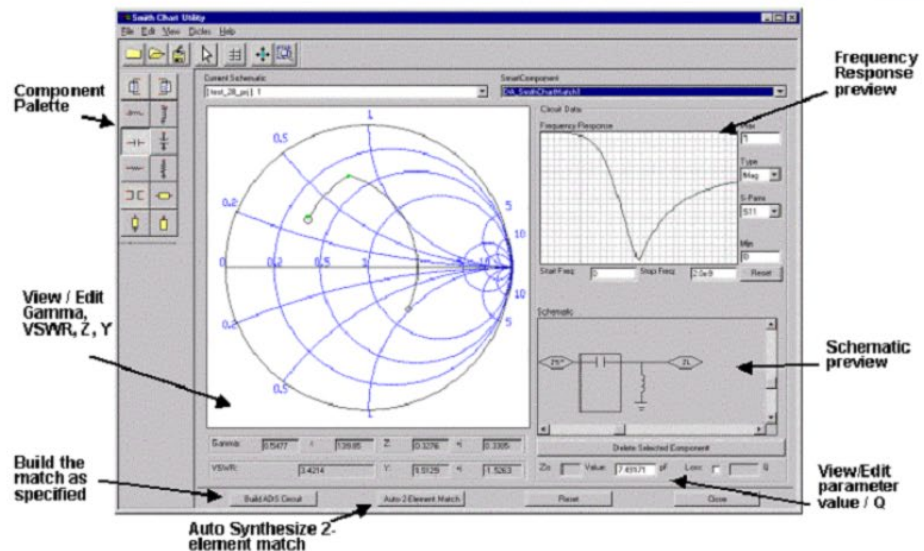Today, a presentation medium in computer-aided design (CAD) software and measuring equipment for displaying the performance of microwave circuits.



Smith Chart: Introduction

Reflection coefficient:

$$\Gamma = \frac{Z_L - R_0}{Z_L + R_0} = |\Gamma|e^{j\theta_\Gamma} = \Gamma_r + j\Gamma_i$$

Normalized load impedance:

$$z_L = \frac{Z_L}{R_0} = \frac{R_L}{R_0} + j\frac{X_L}{R_0} = r + jx$$





r-circles:

$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2$$

x-circles:
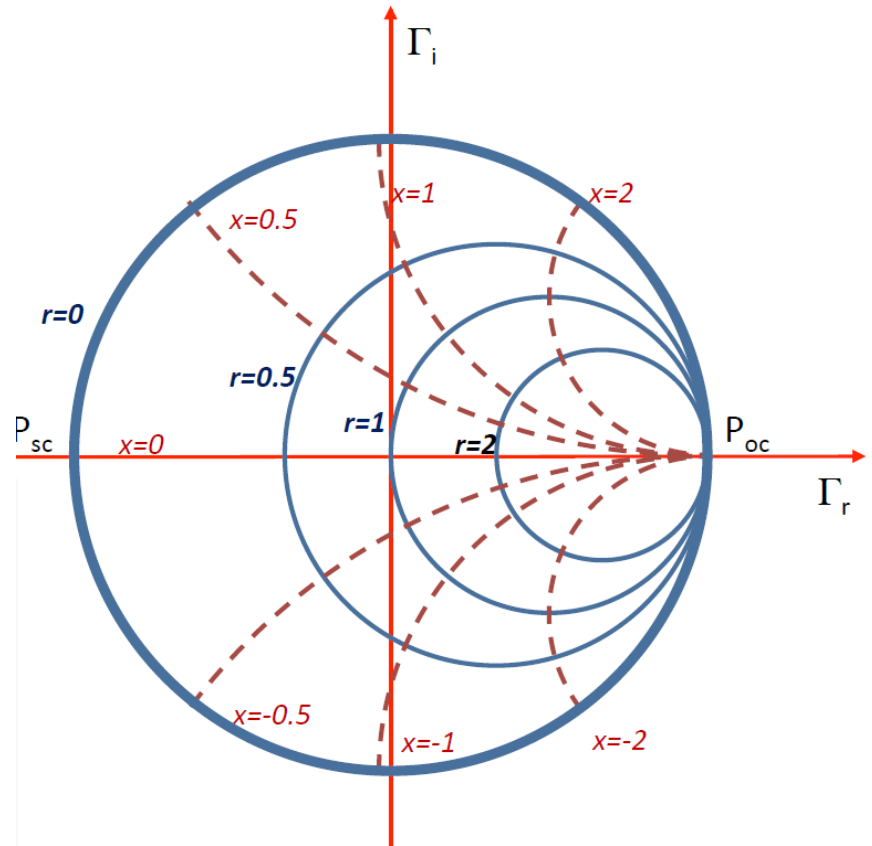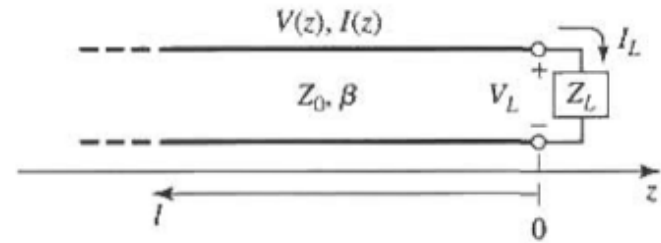
$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$



Smith Chart: Introduction

$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2$$

For the constant r circles:


1. The centers of all the constant r circles are on the horizontal axis – real part of the reflection coefficient.
2. The radius of circles decreases when r increases.
3. All constant r circles pass through the point $\Gamma_r = 1, \Gamma_i = 0$.
4. The normalized resistance $r = \infty$ is at the point $\Gamma_r = 1, \Gamma_i = 0$.

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

For the constant x (partial) circles:

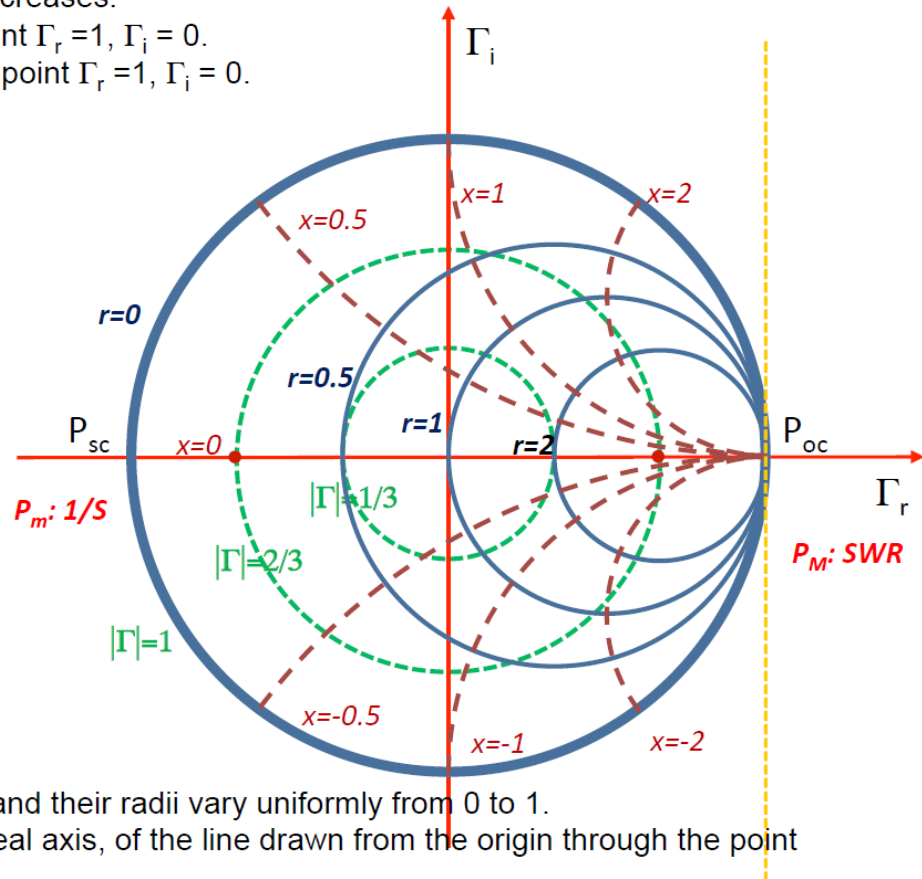1. The centers of all the constant x circles are on the $\Gamma_r = 1$ line. The circles with $x > 0$ (inductive reactance) are above the Γ_r axis; the circles with $x < 0$ (capacitive) are below the Γ_r axis.
2. The radius of circles decreases when absolute value of x increases.
3. The normalized reactances $x = \pm\infty$ are at the point $\Gamma_r = 1, \Gamma_i = 0$

The constant r circles are orthogonal to the constant x circles at every intersection.




1. All $|\Gamma|$ -circles are centered at the origin, and their radii vary uniformly from 0 to 1.
2. The angle, measured from the positive real axis, of the line drawn from the origin through the point representing z_L equals θ_r .
3. The value of the r -circle passing through the intersection of the $|\Gamma|$ -circle and the positive real axis equals the standing-wave ratio S

Smith Chart: Introduction

Examples

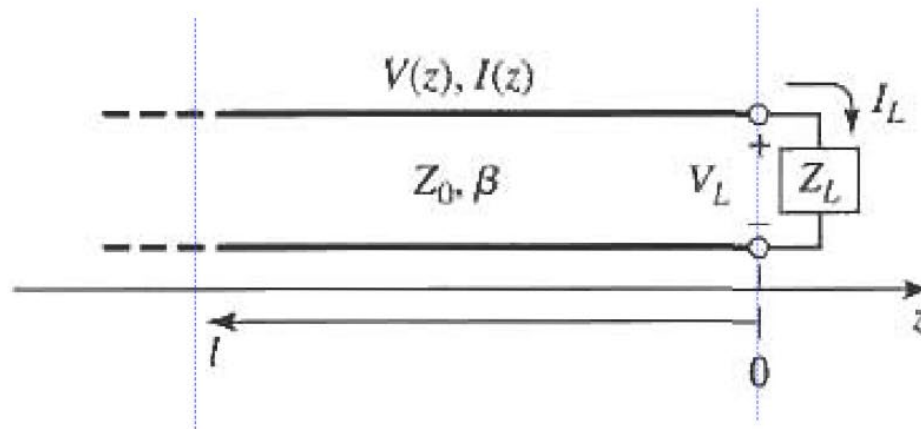EXAMPLE 9–14 A lossless transmission line of length 0.434λ and characteristic impedance $100\ \Omega$ is terminated in an impedance $260 + j180\ \Omega$. Find (a) the voltage reflection coefficient, (b) the standing-wave ratio, (c) the input impedance, and (d) the location of a voltage maximum on the line.



Smith Chart: Introduction

Example 9-14

$$l = 0.434\lambda$$

$$Z_0 = 100\Omega$$

$$Z_L = 260 + j180\Omega$$

Find:

$$\Gamma_0$$

SWR

$$Z_{in}$$

$$l_{max}$$

