


B38DB: Digital Design and Programming

Sequential Logic Design – Controller Examples

Mustafa Suphi Erden

Heriot-Watt University
School of Engineering & Physical Sciences
Electrical, Electronic and Computer Engineering
Room: EM 2.01
Phone: 0131-4514159
E-mail: m.s.erden@hw.ac.uk

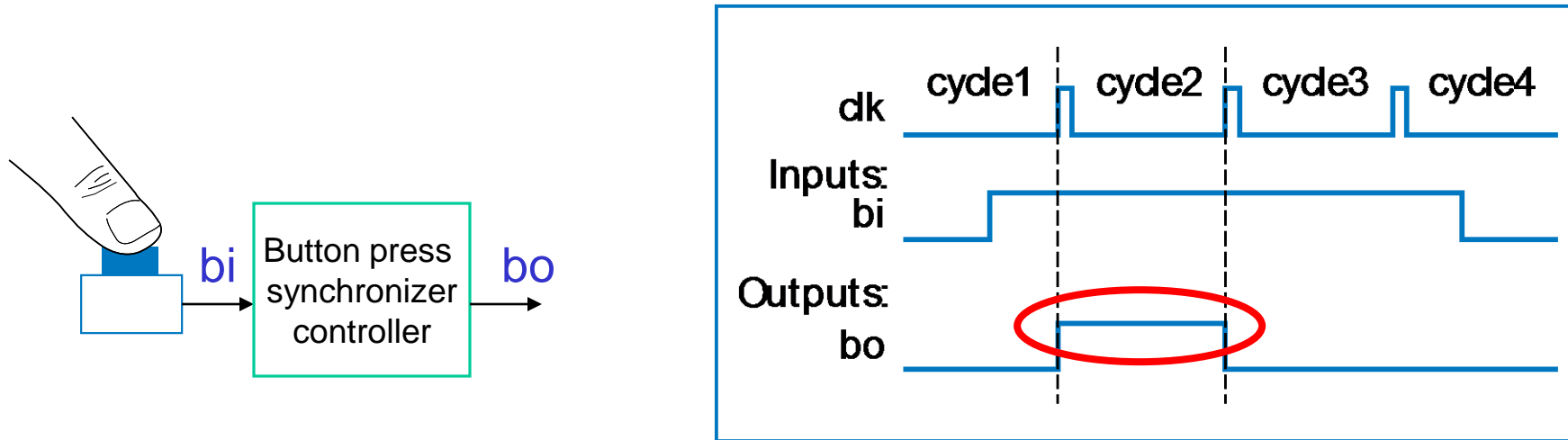
Controller Example: Button Press Synchronizer (1/2)



- We want a simple sequential circuit that converts “button-press” to a single cycle duration, regardless of the length of the time that the button is actually pressed
 - We assumed such an ideal button-press signal in earlier examples, like the button in the laser timer controller


Controller Example: Button Press Synchronizer (2/2)

FSM inputs: bi; FSM outputs: bo

 

Step 1: FSM

FSM inputs: bi; FSM outputs: bo

 


Step 3: Encode states

$$n1 = s1's0bi + s1s0bi$$

$$n0 = s1's0'bi$$


$$bo = s1's0bi' + s1's0bi = s1s0$$

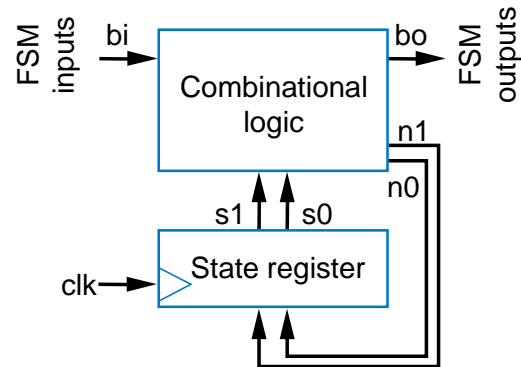

Step 2: Create architecture

	Combinational logic Inputs			Outputs		
	s1	s0	bi	n1	n0	bo
A	0	0	0	0	0	0
	0	0	1	0	1	0
B	0	1	0	0	0	1
	0	1	1	1	0	1
C	1	0	0	0	0	0
	1	0	1	1	0	0
unused	1	1	0	0	0	0
	1	1	1	0	0	0


Step 4: State table

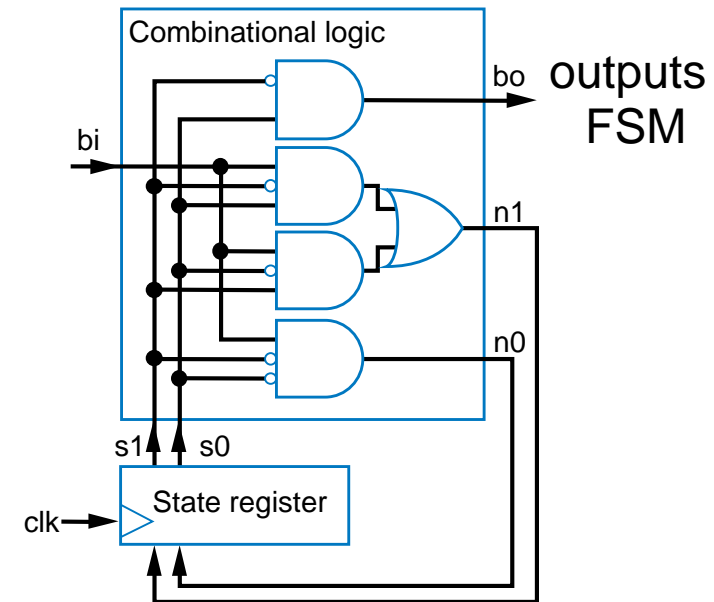


Step 5: Create combinational circuit

Controller Example: Sequence Generator

 
- We want to generate the sequence 0001, 0011, 1100, 1000, (repeats)
 - One binary number for each clock cycle
 - Common examples: to create a pattern with 4 lights, or to control the magnets of a “stepper motor”



Step 1: Create FSM

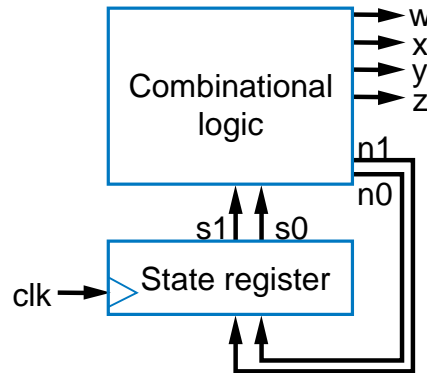

Step 2: Create architecture

 


Step 3: Encode states

	Inputs		Outputs					
	s1	s0	w	x	y	z	n1	n0
A	0	0	0	0	0	1	0	1
B	0	1	0	0	1	1	1	0
C	1	0	1	1	0	0	1	1
D	1	1	1	0	0	0	0	0

Step 4: Create state table
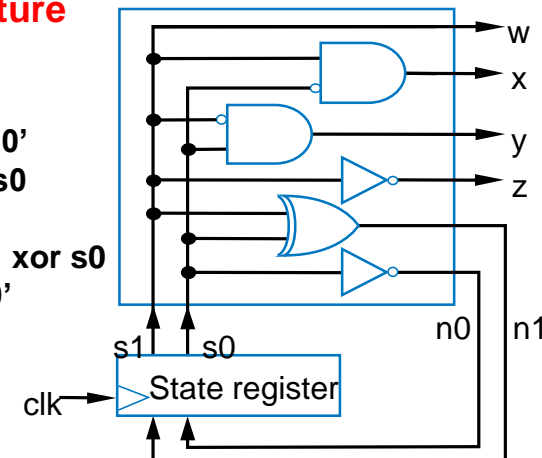
$$\begin{aligned}
 w &= s1 \\
 x &= s1s0' \\
 y &= s1's0 \\
 z &= s1' \\
 n1 &= s1 \text{ xor } s0 \\
 n0 &= s0'
 \end{aligned}$$





Step 5: Create combinational circuit

Controller Example: Secure Car Key (1/2)

- Many new car keys include a tiny computer chip
 - When the car starts, the car's computer (under engine hood) requests the identifier from key
 - The key transmits the identifier
 - If not, the computer shuts off the car


- FSM

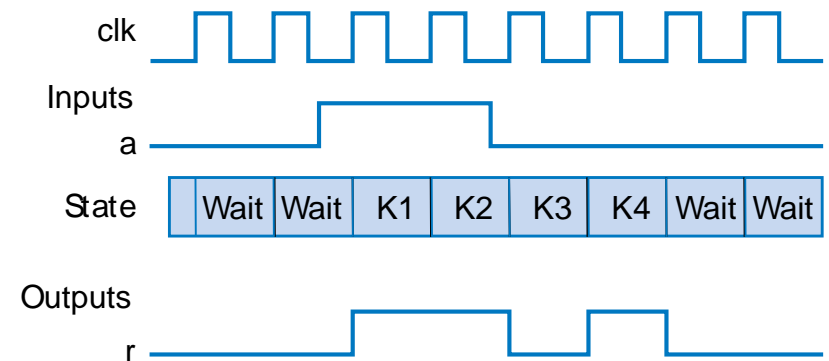 - Wait until the computer requests ID ($a=1$)
- Transmit the ID (in this case, 1101)



Timing diagrams show states and output values for different input waveforms


Controller Example: Secure Car Key (2/2)

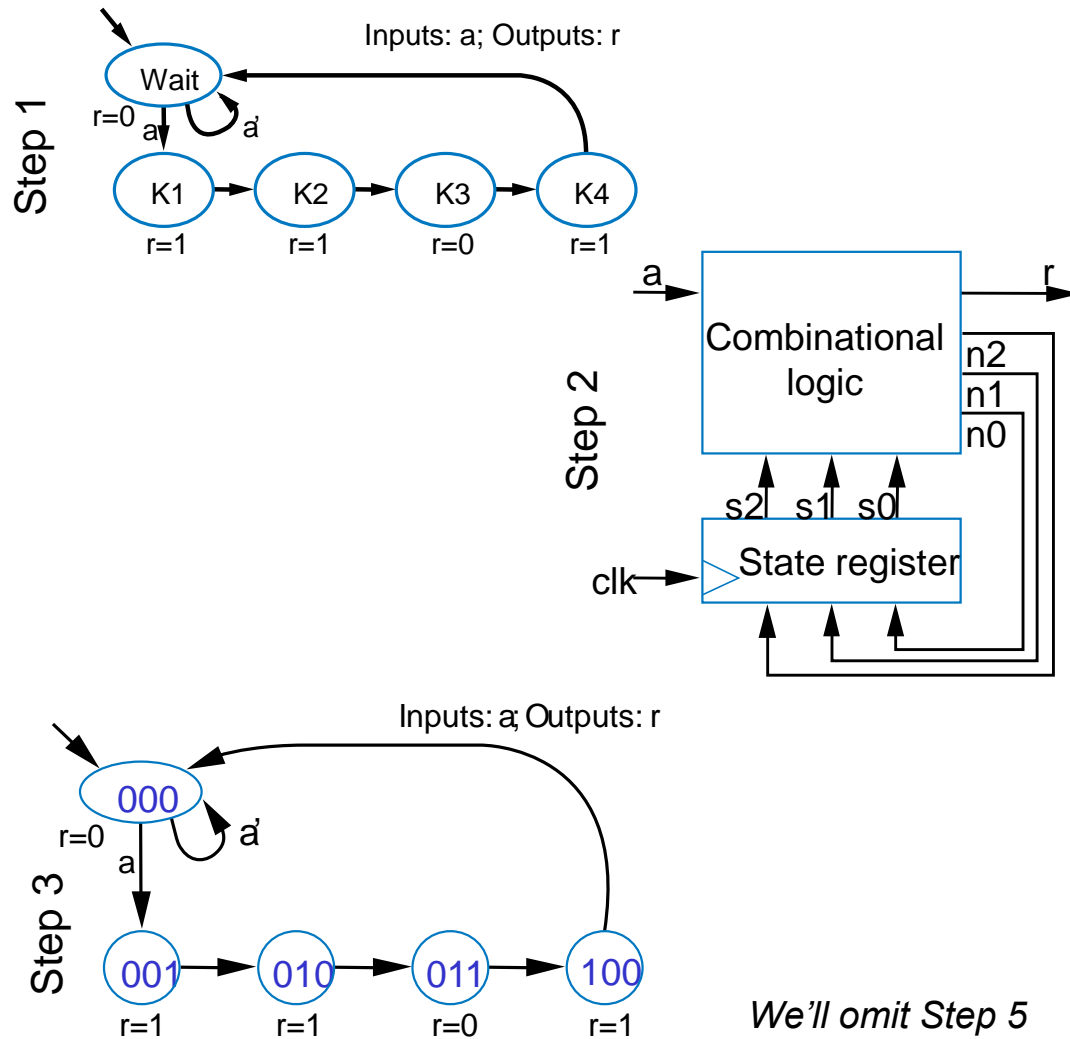

Inputs					Outputs			
	s2	s1	s0	a	r	n2	n1	n0
Wait	0	0	0	0	0	0	0	0
	0	0	0	1	0	0	0	1
K1	0	0	1	0	1	0	1	0
	0	0	1	1	1	0	1	0
K2	0	1	0	0	1	0	1	1
	0	1	0	1	1	0	1	1
K3	0	1	1	0	0	1	0	0
	0	1	1	1	0	1	0	0
K4	1	0	0	0	1	0	0	0
	1	0	0	1	1	0	0	0
Unused	1	0	1	0	0	0	0	0
	1	0	1	1	0	0	0	0
	1	1	0	0	0	0	0	0
	1	1	0	1	0	0	0	0
	1	1	1	0	0	0	0	0
	1	1	1	1	0	0	0	0
	1	1	1	1	0	0	0	0

Step 4

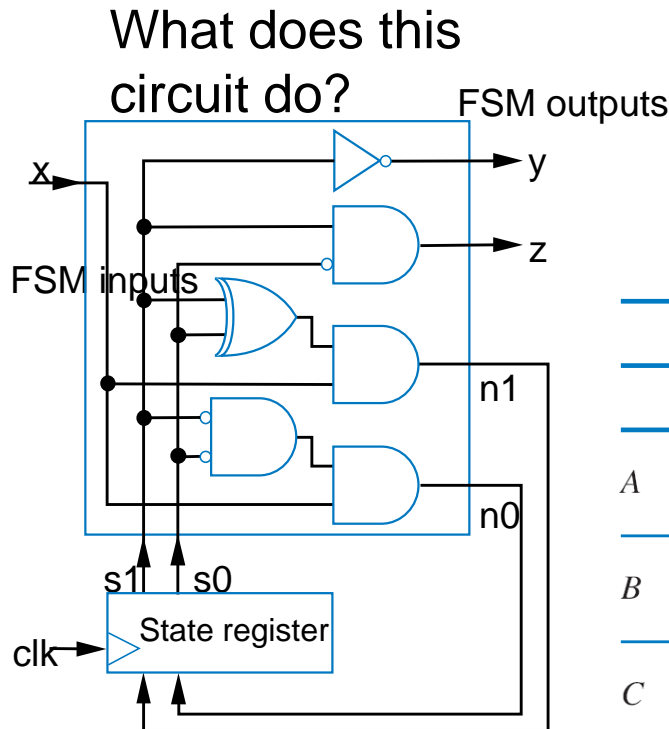Example: Seq. Circuit to FSM (Reverse Engineering)



Work backwards

$$y = s1'$$


$$z = s1s0'$$

$$n1 = (s1 \text{ xor } s0)x$$



$$n0 = (s1' * s0')x$$

	Inputs			Outputs			
	s1	s0	x	n1	n0	y	z
A	0	0	0	0	0	1	0
	0	0	1	0	1	1	0
B	0	1	0	0	0	1	0
	0	1	1	1	0	1	0
C	1	0	0	0	0	0	1
	1	0	1	1	0	0	1
D	1	1	0	0	0	0	0
	1	1	1	0	0	0	0

Pick any state names you want

 



Outputs: y, z

  



states with outputs and transitions

Common Pitfalls Regarding Transition Properties

  - **Non-exclusive transitions:** Only one condition should be true for all transitions leaving a state



  - **Incomplete transitions:** One condition must be true for all transitions leaving a state



Verifying Correct Transition Properties

- We can verify by using Boolean algebra


- Only one condition is true: AND of each condition pair (for transitions leaving a state) should be equal to 0

→ proves that more than one output can never be simultaneously true

- At least one condition is true: OR of all conditions of the transitions leaving a state should be equal to 1

→ proves that at least one condition is true

- Example

 

Answer:

$$\begin{aligned} & a * a'b \\ &= (a * a') * b \\ &= 0 * b \\ &= 0 \\ &\text{OK!} \end{aligned}$$

$$\begin{aligned} & a + a'b \\ &= a*(1+b) + a'b \\ &= a + ab + a'b \\ &= a + (a+a')b \\ &= a + b \end{aligned}$$

Fails! Might not be 1
(i.e., $a=0, b=0$)


Q: Prove whether:

- * Only one condition is true (AND of each pair is always 0)
- * There is a condition which is true (OR of all transitions is always 1)

Evidence that Pitfall is Common

■ Recall the code detector FSM

 - We “fixed” a problem with the transition conditions
- Do the transitions satisfy the two requirements?
 - Consider transitions of state *Start*, and the “only one true” property



$$\begin{aligned} ar * a' \\ = (a * a')r \\ = 0 \end{aligned}$$

$$\begin{aligned} a' * a(r'+b+g) \\ = 0 * r \\ = 0 \end{aligned}$$

$$\begin{aligned} ar * a(r'+b+g) \\ = (a' * a) * (r' + b + g) &= 0 * (r' + b + g) \\ = (a * a) * r * (r' + b + g) &= a * r * (r' + b + g) \\ = arr' + arb + arg \\ = 0 + arb + arg \\ = arb + arg \\ = ar(b+g) \end{aligned}$$

Fails! Means that two of Start's transitions could be true at the same time

Intuitively: press the red and blue buttons at the same time: conditions ar , and $a(r'+b+g)$ will be both true. Which one should be taken?

Q: How to solve?

A: ar should be $arb'g'$ (likewise for ab , ag , ar)

Note: As evidence for that the pitfall is common, we admit that the mistake was not intentional.
A reviewer of the book caught it.



Simplifying Notations

■ FSMs

- Assume any unassigned output implicitly assigned to 0



■ Sequential circuits

  - Assume unconnected clock inputs to be connected to the same external clock



Flip-Flop Set and Reset Inputs

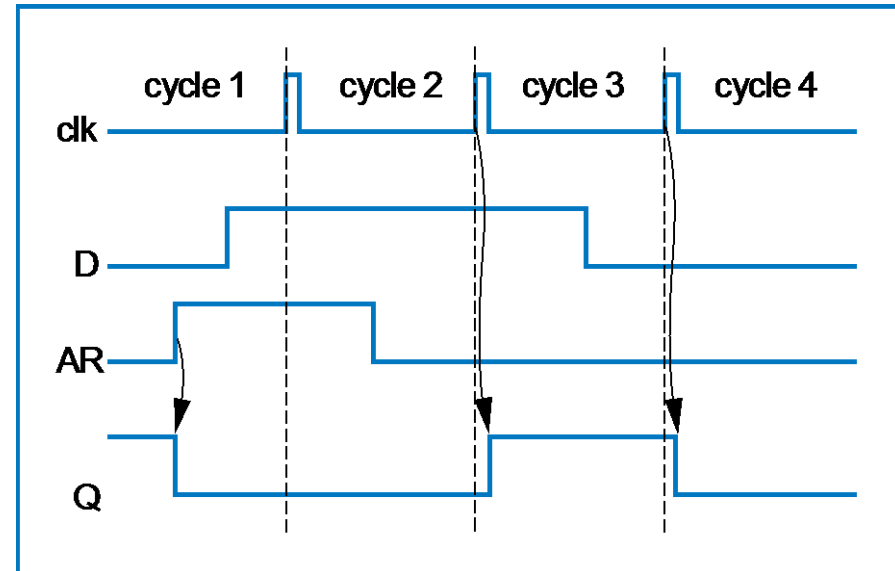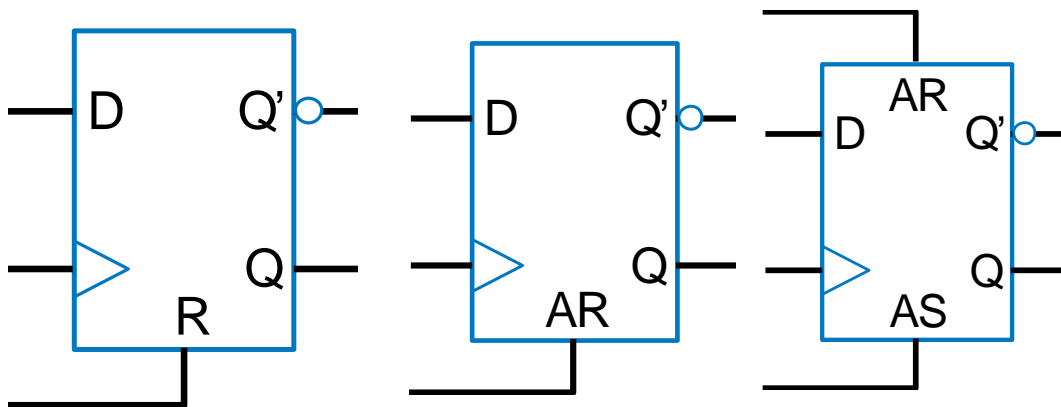- Some flip-flops have additional inputs
 - Synchronous reset: clears Q to 0 on the next clock edge
 - Synchronous set: sets Q to 1 on the next clock edge
 - Asynchronous reset: clears Q to 0 immediately (not dependent on the clock edge)
 - Example timing diagram shown
 - Asynchronous set: sets Q to 1 immediately



Initial State of a Controller

- All our FSMs had initial state
 - But our sequential circuit designs did not
 - Can we accomplish having an initial state by using flip-flops with reset/set inputs
 - Shown circuit initializes the flip-flops to the **state 01**

