

B38DB: Digital Design and Programming

Datapath Components – Adders and Comparators

Mustafa Suphi Erden

Heriot-Watt University
School of Engineering & Physical Sciences
Electrical, Electronic and Computer Engineering
Room: EM 2.01
Phone: 0131-4514159
E-mail: m.s.erden@hw.ac.uk

Adders


- Adds two N-bit binary numbers
 - 2-bit adder: adds two 2-bit numbers, outputs 3-bit result
 - e.g., $01 + 11 = 100$ ($1 + 3 = 4$)
- We can design using combinational design process, but doesn't work well for reasonable-size N.
 - Why not?

Inputs				Outputs		
a1	a0	b1	b0	c	s1	s0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Why Adders Aren't Built Using Standard Combinational Design Process

- Truth table too big

 
- 2-bit adder's truth table shown
 - Has $2^{(2+2)} = 16$ rows
- 8-bit adder: $2^{(8+8)} = 65,536$ rows
- 16-bit adder: $2^{(16+16)} = \sim 4$ billion rows
- 32-bit adder: ...
- Plot shows number of transistors for N-bit adders, using state-of-the-art automated combinational design tool



Inputs				Outputs		
a1	a0	b1	b0	c	s1	s0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0


Alternative Method to Design an Adder: Imitate Adding by Hand (1/2)

 - Alternative adder design: mimic how people do addition by hand
- One column at a time
 - Compute sum, add carry to next column




Alternative Method to Design an Adder: Imitate Adding by Hand (2/2)

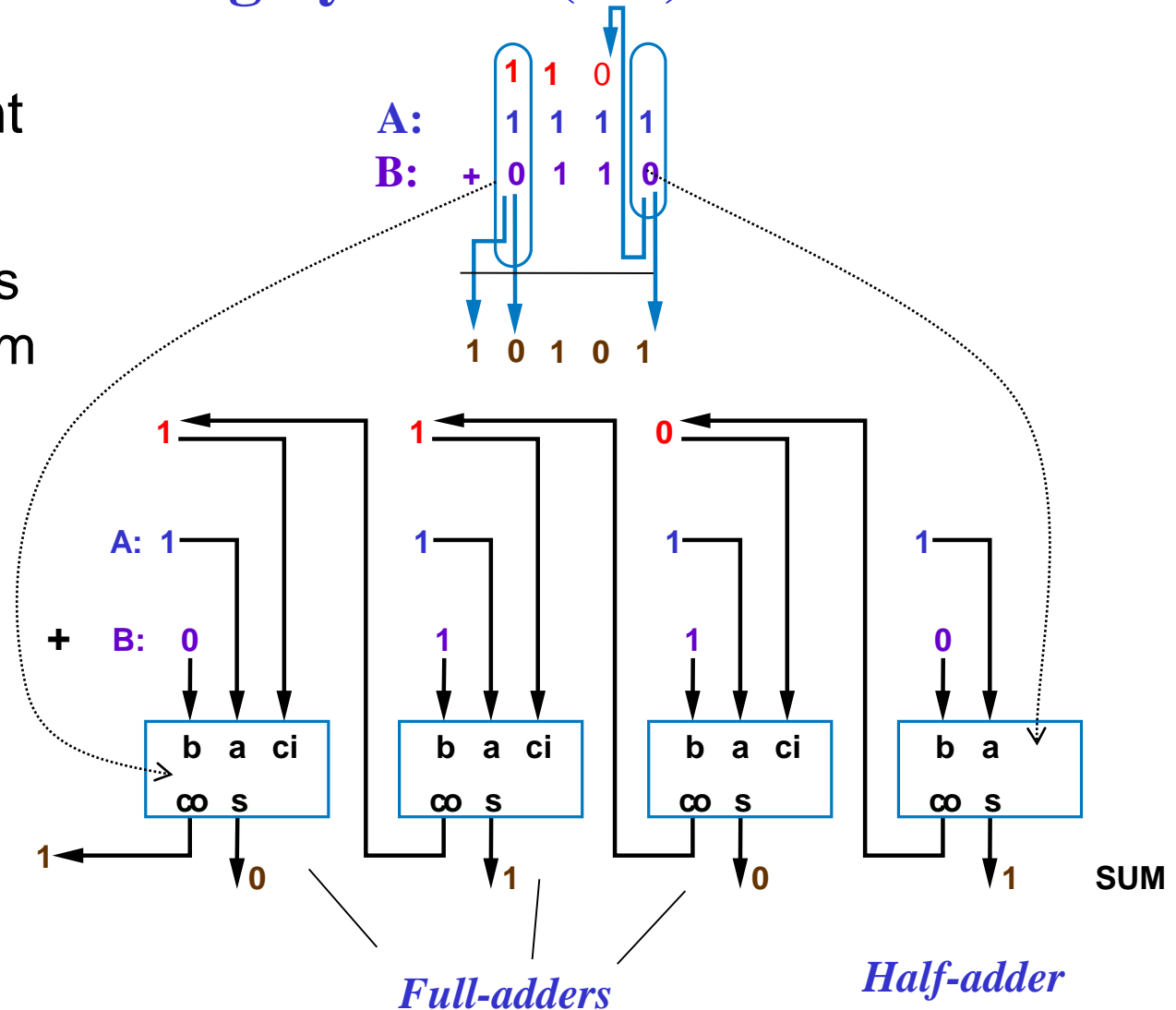- Create a component for each column
 - Add that column's bits, generate sum and carry bits



Half-Adder

 - **Half-adder**: Adds 2 bits, generates sum and carry
- Design using combinational design process as we did before



Step 1: Capture the function


Inputs		Outputs	
a	b	co	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Step 2: Convert to equations

$$co = ab$$


$$s = a'b + ab' \text{ (same as } s = a \text{ xor } b; a \oplus b)$$

Step 3: Create the circuit

 

Full-Adder

 - **Full-adder:** Adds 3 bits, generates sum and carry
- Design using combinational design process



Step 1: Capture the function


Inputs			Outputs	
a	b	ci	co	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Step 2: Convert to equations

$$\begin{aligned} co &= a'bc + ab'c + abc' + abc \\ co &= a'bc + abc + ab'c + abc + abc' \\ &+ abc \\ co &= (a' + a)bc + (b' + b)ac + (c' + c)ab \\ co &= bc + ac + ab \end{aligned}$$


$$\begin{aligned} s &= a'b'c + a'bc' + ab'c' + abc \\ s &= a'(b'c + bc') + a(b'c' + bc) \\ s &= a'(b \text{ xor } c)' + a(b \text{ xor } c) \\ s &= a \text{ xor } b \text{ xor } c \end{aligned}$$

Step 3: Create the circuit

 


Carry-Ripple Adder (1/2)

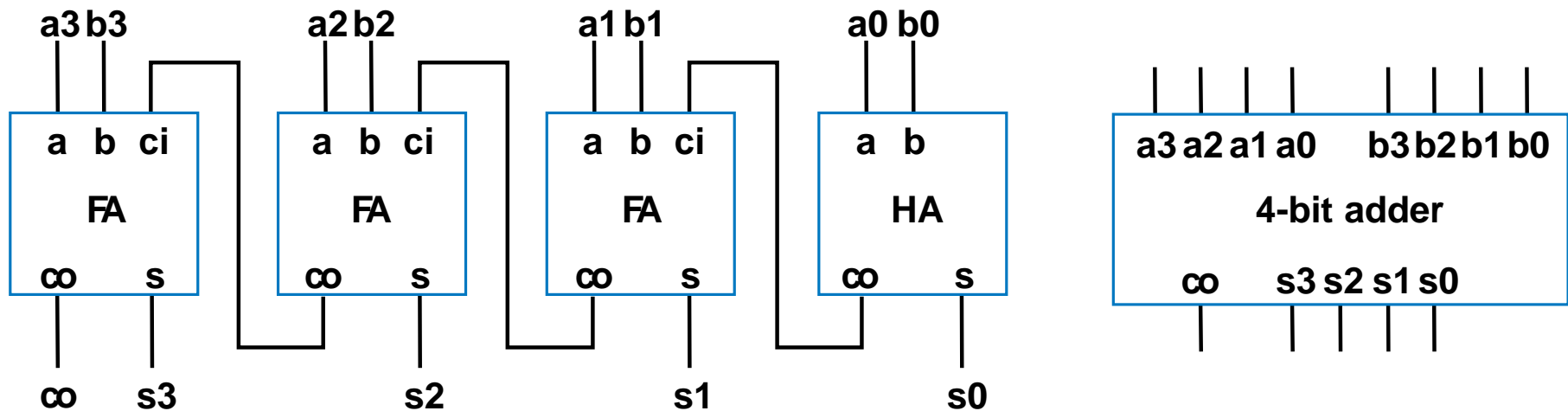- Using half-adder and full-adders, we can build an adder that adds like we would do by hand.
- Called a *carry-ripple adder*
 - 4-bit adder shown: Adds two 4-bit numbers, generates 5-bit output
 - 5-bit output can be considered 4-bit “sum” plus 1-bit “carry out”
 - Can easily build any size adder




Carry-Ripple Adder (2/2)

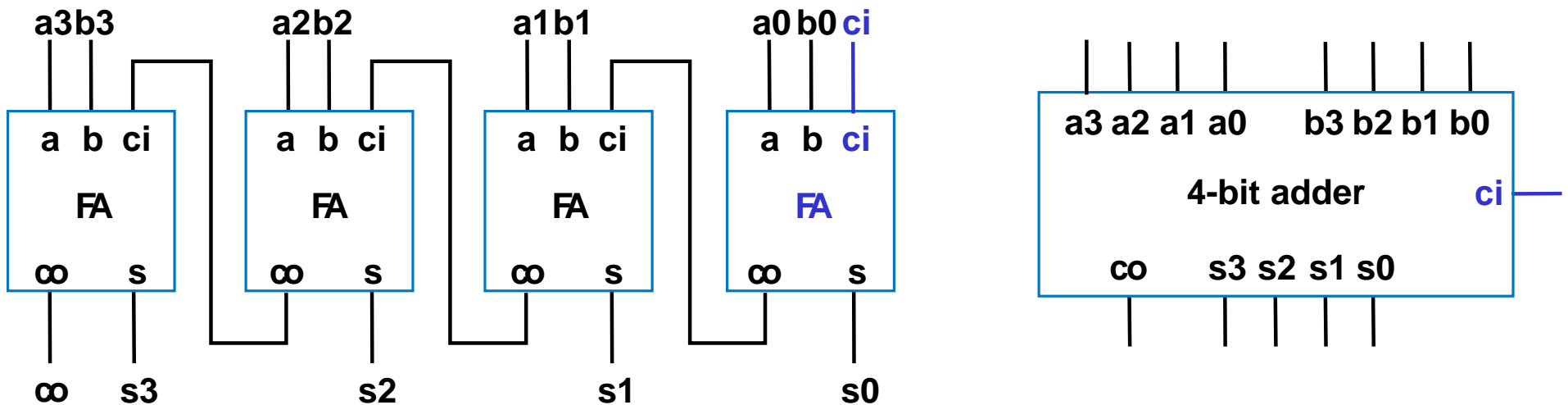- Using a full-adder instead of a half-adder for the first bit, we can include a “carry in” bit in the addition
 - Useful to connect smaller adders to form bigger adders




Cascading Adders

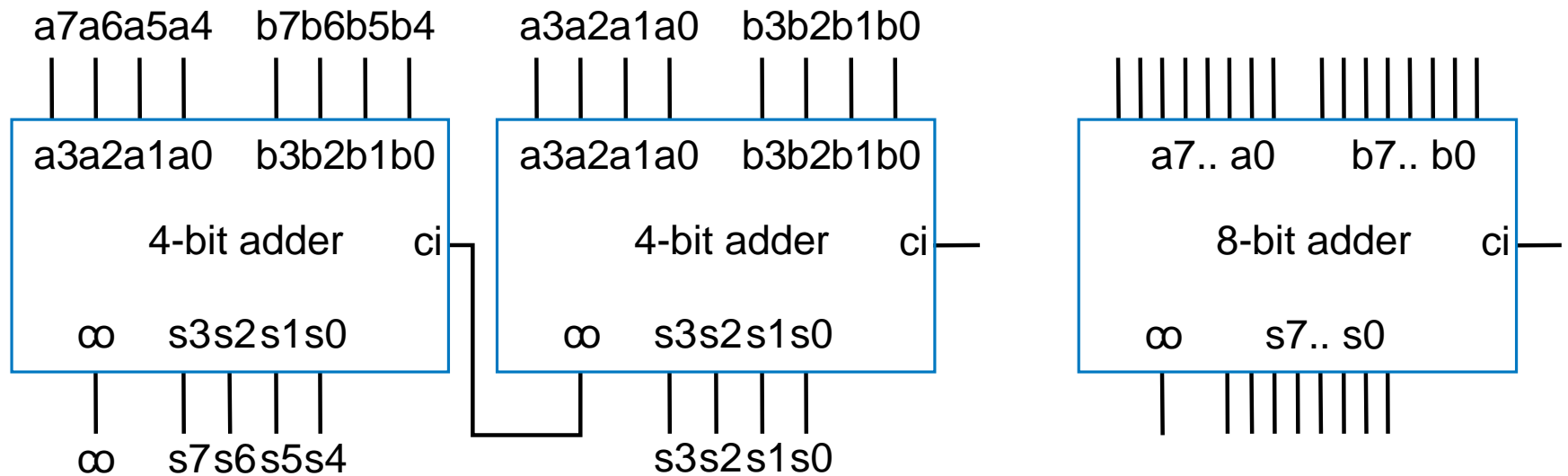


Adder Example: DIP-Switch-Based Adding Calculator (1/2)

 - Calculator that adds two 8-bit binary numbers, specified using DIP switches




Adder Example: DIP-Switch-Based Adding Calculator (2/2)

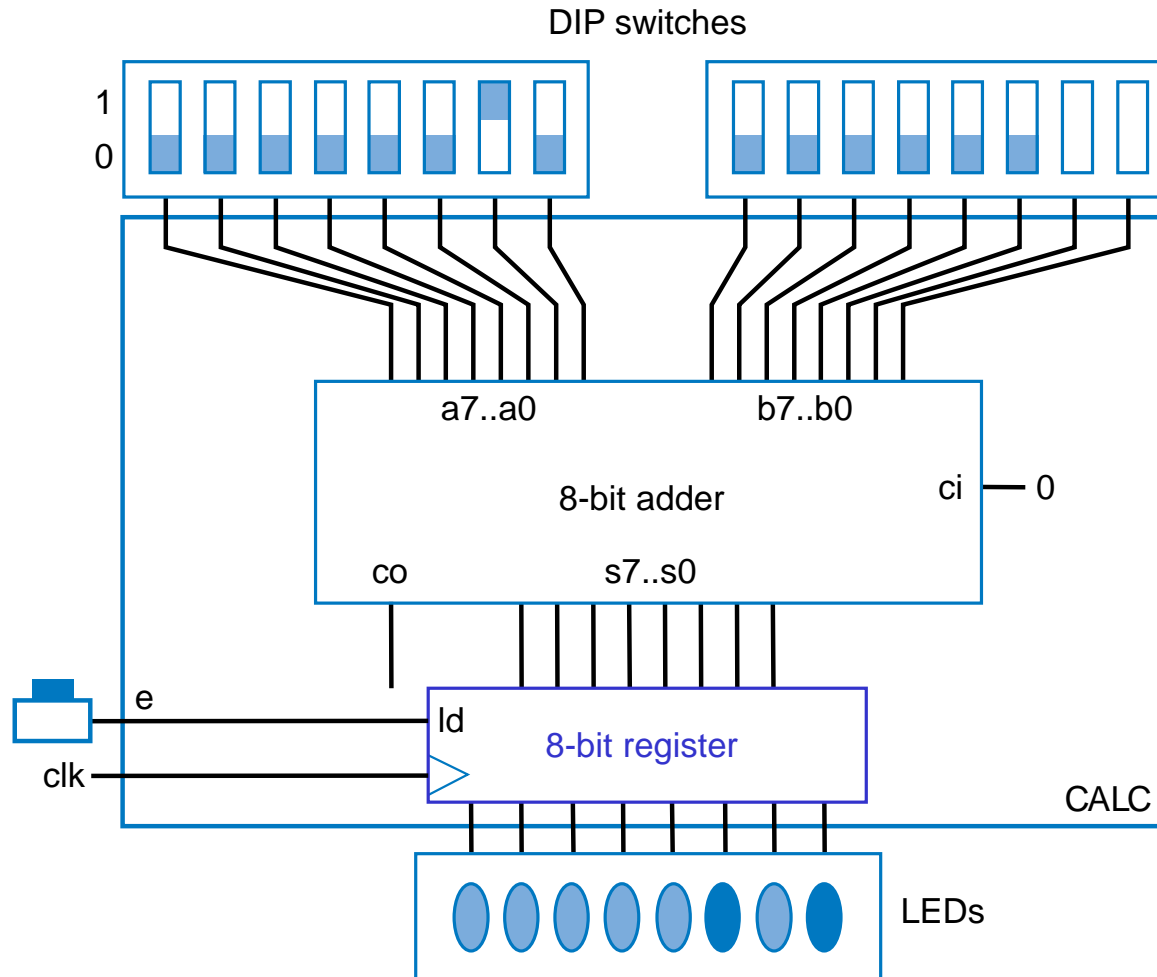- To prevent spurious values from appearing at the output while data propagation through the carry-ripple adder's gates, we can place a register at the output.



Comparators

 - ***N-bit equality comparator***: Outputs 1 if two N-bit numbers are equal
 - 4-bit equality comparator with inputs A and B
 - Recall that XNOR outputs 1 if its two input bits are the same
 - $eq = (a3 \otimes b3) * (a2 \otimes b2) * (a1 \otimes b1) * (a0 \otimes b0)$



Magnitude Comparator (1/3)

- ***N-bit magnitude comparator***: Indicates whether

$A > B$, $A = B$, or $A < B$, for its two N-bit inputs A and B

- How to design?

A=1011 B=1001

1011 1001 Equal



1011 1001 Equal

1011 1001 Unequal


So $A > B$

Magnitude Comparator (2/3)

 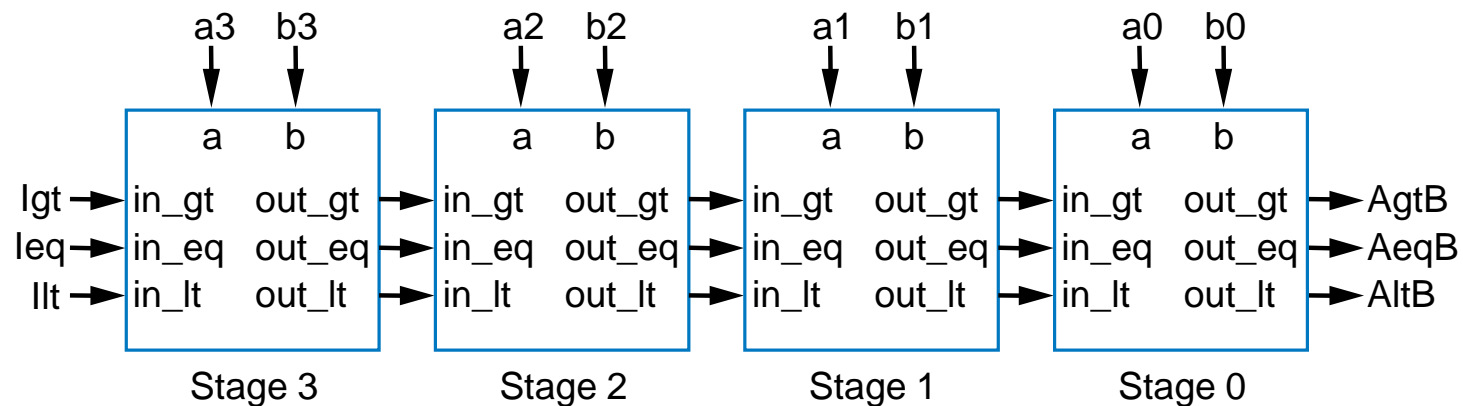- Start at left, compare each bit pair, pass results to the right
- Each stage has 3 inputs indicating results of higher stage, passes results to lower stage



Magnitude Comparator (3/3)

 

■ Each stage:

- $\text{out_gt} = \text{in_gt} \text{ OR } (\text{in_eq} \text{ AND } a \text{ AND } b')$
- $\text{out_lt} = \text{in_lt} \text{ OR } (\text{in_eq} \text{ AND } a' \text{ AND } b)$
- $\text{out_eq} = \text{in_eq} \text{ AND } (a \text{ XNOR } b)$
- Simple circuit inside each stage, just a few gates (not shown)

Magnitude Comparator Example: Minimum of Two Numbers

- Design a combinational component that computes the minimum of two 8-bit numbers
 - Solution: Use 8-bit magnitude comparator and 8-bit 2x1 mux
 - If $A < B$, pass A through mux. Else, pass B.

