



# **B38DB: Digital Design and Programming Datapath Components – Subtractor**

**Mustafa Suphi Erden**

Heriot-Watt University  
School of Engineering & Physical Sciences  
Electrical, Electronic and Computer Engineering  
Room: EM 2.01  
Phone: 0131-4514159  
E-mail: [m.s.erden@hw.ac.uk](mailto:m.s.erden@hw.ac.uk)

 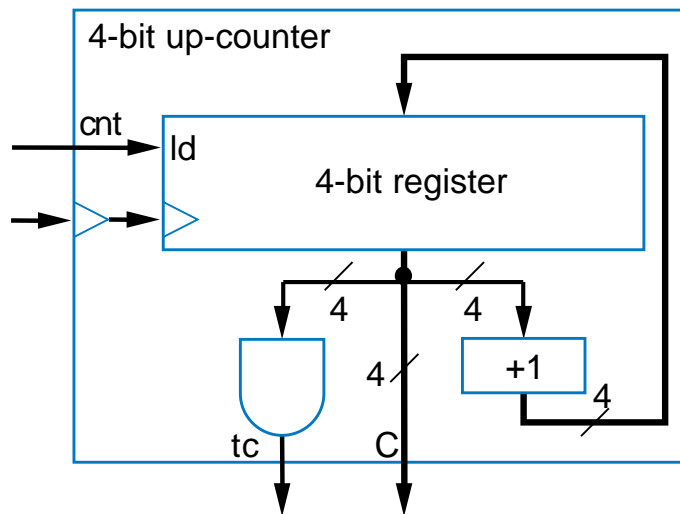
# Counters

- ***N-bit up-counter***: N-bit register that can increment (add 1) to its own value on each clock cycle
  - 0000, 0001, 0010, 0011, ..., 1110, 1111, 0000
  - Note how count “rolls over” from 1111 to 0000
    - Terminal (last) count, tc, equals 1 during value just before rollover
- Internal design
  - Register, incrementer, N-input AND gate


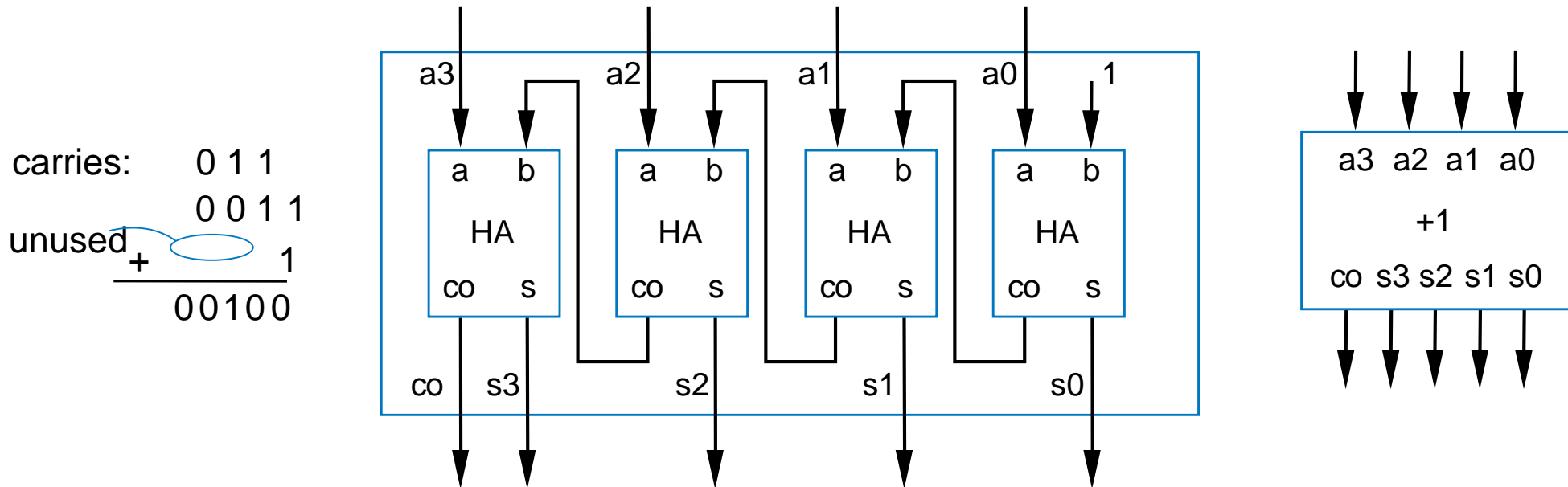
# Incrementer

- We could use carry-ripple adder with B input set to 00...001
  - But when adding 00...001 to another number, the leading 0's obviously don't need to be considered -- so just two bits being added per column
- Use half-adders (adds two bits) rather than full-adders (adds three bits)




**Similarly, implement a decrementer with a Half-Subtractor!**

## Counter Example:
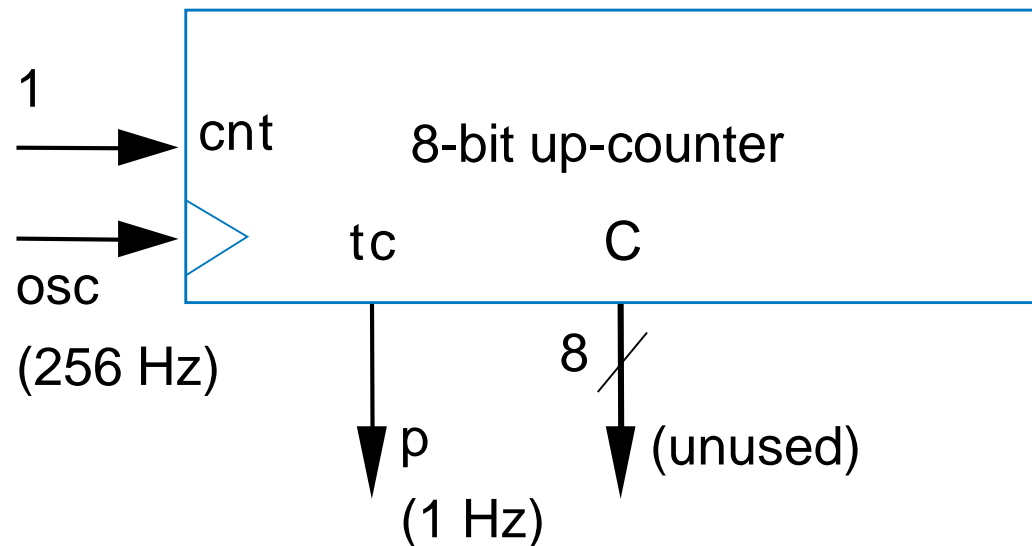
### 1 Hz Pulse Generator Using 256 Hz Oscillator


- Suppose we have **256 Hz** oscillator, but we want **1 Hz** pulses
  - 1 Hz is 1 pulse per second



- 8-bit up-counter, uses tc output as pulse
  - Counts from 0 to 255 (256 counts), so pulses tc every 256 cycles


## B38DB: Digital Design and Programming
 
### Datapath Components – Subtractor and Counters



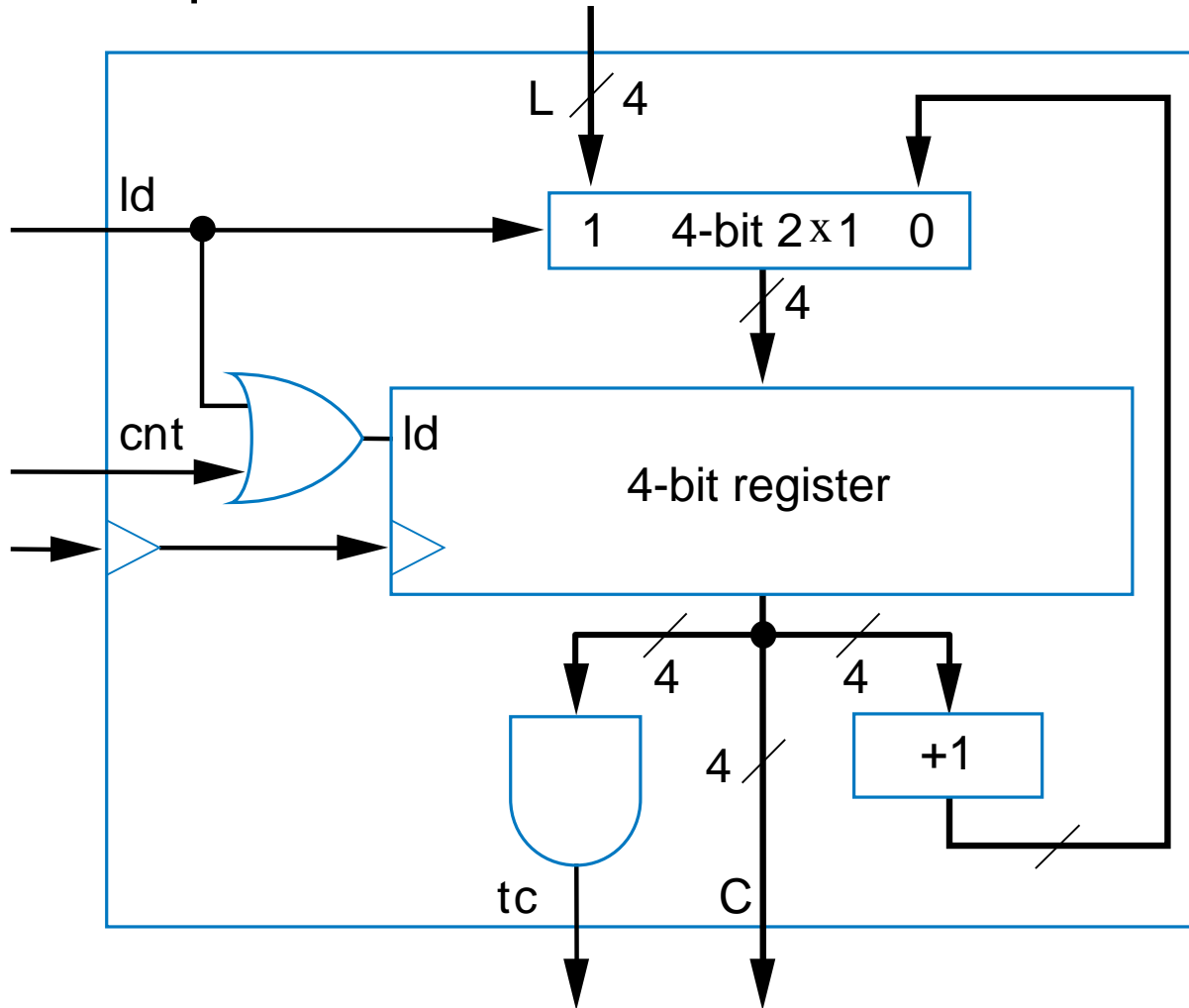
# Counter with Parallel Load

- Up-counter that can be loaded with external value




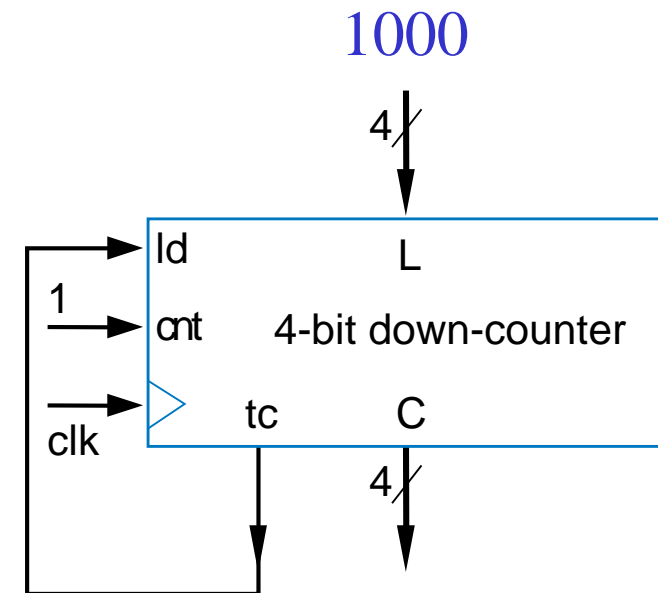- Down-counter that can be loaded with external value


 
# Counter Example: 1 Hz Pulse Generator from 60 Hz Clock

- U.S. electricity standard uses 60 Hz signal
- Use 6-bit up-counter
  - Can count from 0 to 63
  - Create simple logic to detect 59 (for 60 counts)
    - Use to clear the counter back to 0 (or to load 0)



# Representing Negative Numbers: Two's Complement

- We can build a subtractor as we built a carry-ripple adder; but we do not need to!
- How to represent negative numbers in binary?
- Signed-magnitude
  - Use leftmost bit for sign bit
    - So -5 would be:  
1101 using four bits  
10000101 using eight bits
- Better way: Two's complement
  - Big advantage: Allows us to perform **subtraction using addition**
  - Thus, **no need for a separate subtractor component!**




# Ten's Complement (1/2)

- Before introducing two's complement, let's consider ten's complement
  - But, be aware that computers DO NOT USE TEN'S COMPLEMENT. Introduced for intuition only.
  - Complements of each base ten number are shown on the right
    - Complement is the number that when added it gives the result 10

1	→	9
2	→	8
3	→	7
4	→	6
5	→	5
6	→	4
7	→	3
8	→	2
9	→	1
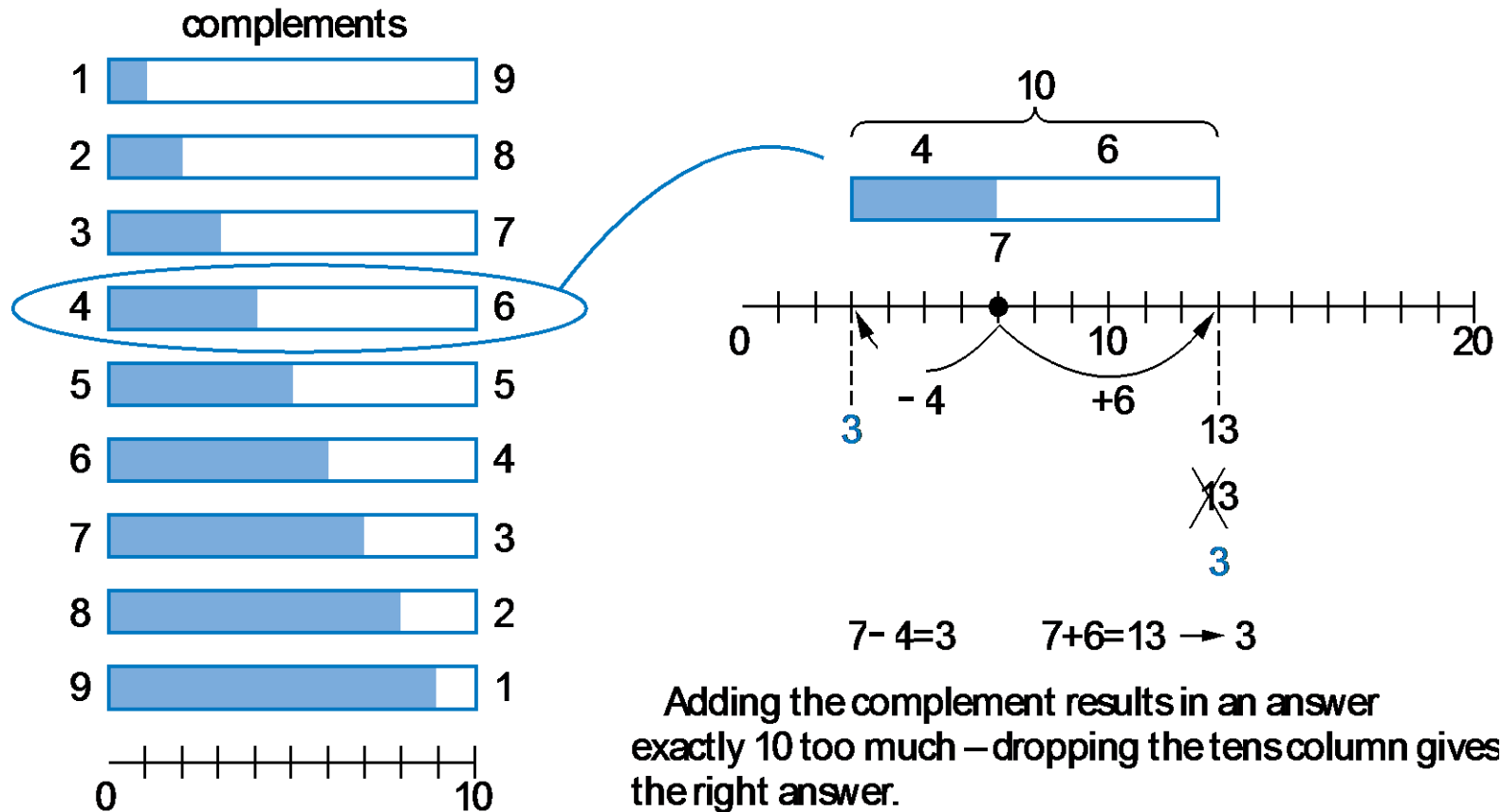
## Ten's Complement (2/2)

- Instead of subtracting a number, adding its complement results in an answer with exactly 10 larger than what it should be
- So just drop the 1 → results in subtracting using addition only



## Two's Complement is Easy to Compute: Just Invert Bits and Add 1

- Two's complement of 011 is 101, because  $011 + 101$  is 1000
- Could compute complement of 011 as  $1000 - 011 = 101$
- **Easier method: Just invert all the bits, and add 1**
- The complement of 011 is  $100+1 = 101$  – it works!

Q: What is the two's complement of 0101?    A:  $1010+1=1011$   
(check:  $0101+1011=10000$ )

Q: What is the two's complement of 0011?    A:  $1100+1=1101$

# Two's Complement Subtractor Built with an Adder


- Using two's complement

$$A - B = A + (-B)$$

$$= A + (\text{two's complement of } B)$$


$$= A + \text{invert\_bits}(B) + 1$$

 - Build a subtractor using an adder, inverting B's bits, and setting carry-in to 1:


 
# Adder/Subtractor

- Adder/subtractor: control input determines whether add or subtract
  - Can use 2x1 mux – sub input passes either B or inverted B
  - Alternatively, can use XOR gates – if sub input is 0, B's bits pass through; if sub input is 1, XORs invert B's bits



## Extra information: Overflow

- Sometimes the result can not be represented with given number of bits:
  - Too large magnitude of either positive or negative value
  - e.g., 4-bit two's complement addition of  $0111+0001$  ( $7+1=8$ ). But 4-bit two's complement can't represent number  $>7$ 
    - $0111+0001 = 1000$  WRONG answer, 1000 in two's complement is -8, not +8
  - Adder/subtractor should indicate when overflow has occurred, so that the result can be discarded.

# Detecting Overflow

- Assuming 4-bit two's complement numbers, can detect overflow by detecting when the two numbers' sign bits are the same but are different from the result's sign bit
  - If the two numbers' sign bits are different, overflow is impossible
    - Adding a positive and negative can't exceed largest magnitude positive or negative
- Simple circuit
  - $\text{overflow} = a_3'b_3's_3 + a_3b_3s_3'$
  - Include "overflow" output bit on adder/subtractor

sign bits

<div>0 1 1 1</div> <div>+0 0 0 1</div> <div>1 0 0 0</div> <div>overflow</div> <div>(a)</div>	<div>1 1 1 1</div> <div>+1 0 0 0</div> <div>0 1 1 1</div> <div>overflow</div> <div>(b)</div>	<div>1 0 0 0</div> <div>+0 1 1 1</div> <div>1 1 1 1</div> <div>no overflow</div> <div>(c)</div>
--	--	---

If the numbers' sign bits have the same value, which differs from the result's sign bit, overflow has occurred.